

Avery Juwan T. Brillantes - 862243108

Thong Thach - 862224662

Lab 5 - Switch-Mode DC-DC Converters

Lab Section 021

TA's Name: Zijin Pan

Introduction:

The objective of this lab is to understand the principles of operation of buck and buck-boost DC-DC converters. We will learn how discontinuous current mode (DCM) affects converters. We will know how to design DC-DC converters that operate in continuous current mode (CCM). We will learn how the non-linear switching operation can be replaced by the linear average CCM-DCM modeling, and its advantages and disadvantages. We will understand the need for system feedback control in the design/development of switch-mode regulators.

Theory:

PART 1: Buck Converter

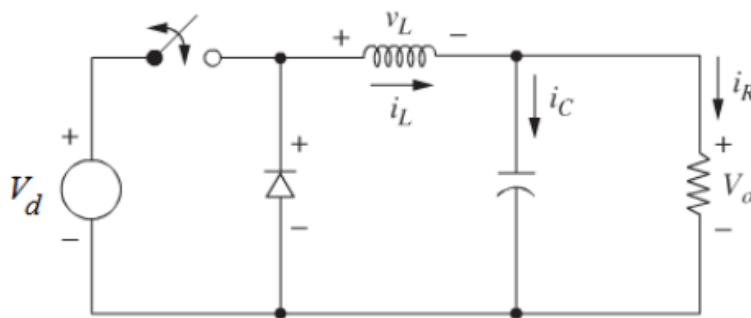


Figure 1.1 The Buck converter

A buck converter produces a DC voltage V_o less or equal to the input voltage V_d depending on the duty cycle of the switch D . This means that it steps-down voltage. The average capacitor current is zero so, the average output current is equal to the average inductor current, $I_o = I_R = I_L$. The average voltage across the inductor is zero, so the average output voltage is equal to the average capacitor voltage $V_o = V_C$. It can operate in continuous current mode (CCM) (I_L is never 0) or discontinuous current mode (DCM) (I_L is 0 for some part).

CCM Equations

Output Voltage

$$(1.1) \quad V_o = DV_d$$

Maximum and Minimum inductor current

$$(1.2) \quad I_{\max} = V_o \left(\frac{1}{R} + \frac{1-D}{2Lf} \right)$$

$$(1.3) \quad I_{\min} = V_o \left(\frac{1}{R} - \frac{1-D}{2Lf} \right)$$

Inductor

$$(1.6) \quad L = \frac{V_o (1-D)}{\Delta i_L f}$$

Ripple Voltage

$$(1.7) \quad \frac{\Delta V_o}{V_o} = \frac{1-D}{8LCf^2}$$

Capacitor

$$(1.8) \quad C = \frac{1-D}{8L \left(\frac{\Delta V_o}{V_o} \right) f^2}$$

Boundary between CCM and DCM

$$(1.4) \quad I_{\min} = 0 = V_o \left(\frac{1}{R} - \frac{1-D}{2Lf} \right)$$

$$(Lf)_{\min} = \frac{(1-D)R}{2}$$

$$(1.5) \quad L_{\min} = \frac{(1-D)R}{2f}$$

DCM Equations

Output Voltage

$$(1.9) \quad V_o = V_d \frac{2D}{D + \sqrt{D^2 + 8 \frac{Lf}{R}}}$$

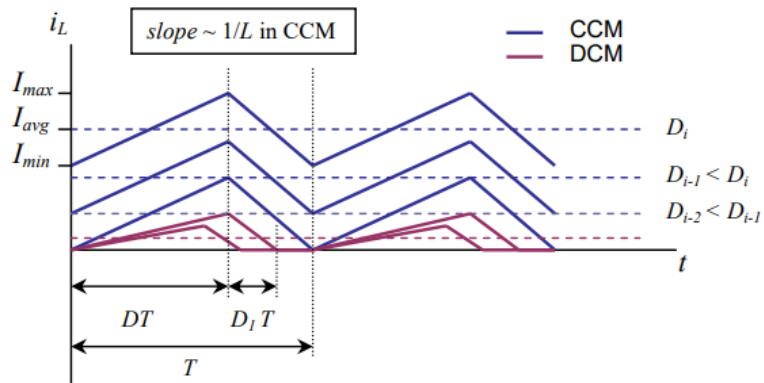


Figure 1.2 Inductor current in CCM and DCM as a function of duty cycle D

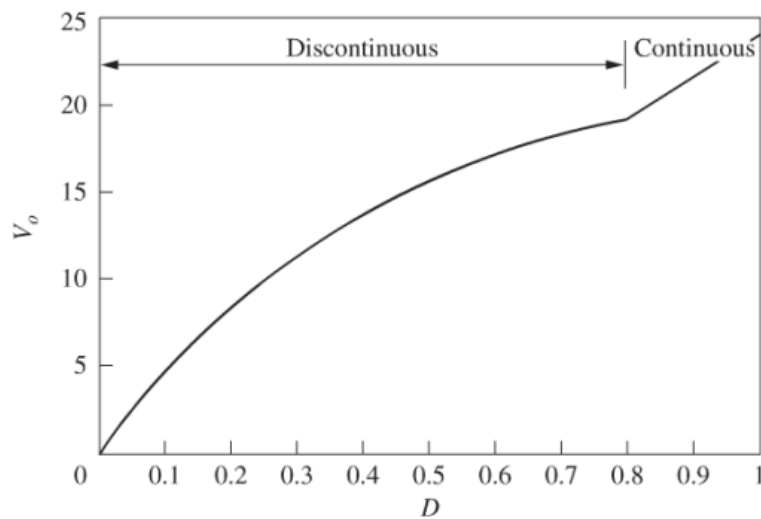


Figure 1.3 The output buck converter voltage vs duty cycle

As a note, ideal inductors, capacitors, and switches do not consume power and power is only consumed by the load R . Ideally, the power efficiency of switching power supplies η is 100%. In reality we can expect 96-98%.

Power Conversion Efficiency

$$(1.10) \quad \eta = \frac{\text{power consumed by the load}}{\text{power generated}} \times 100\% = \left| \frac{P_{out}}{P_{in}} \right| \times 100\%$$

PART 2: Buck-Boost Converters

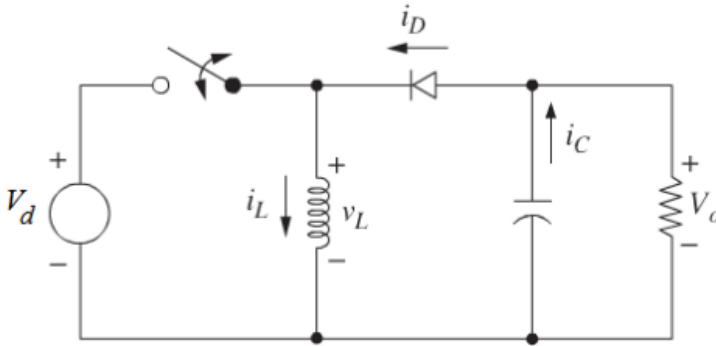


Figure 2.1 The Buck-Boost converter

Buck-Boost Converters allow either a step-up or a step-down of the output voltage depending on the value of the duty cycle. The output voltage is the opposite polarity of the input voltage. If the duty cycle is greater than 0.5 then the output voltage is stepped up. If the duty cycle is less than 0.5 then the output voltage is stepped down.

Output Voltage

$$(2.1) \quad V_o = -V_d \frac{D}{1-D}$$

Duty cycle in terms of input and output voltage

$$(2.2) \quad D = \frac{|V_o|}{V_d + |V_o|}$$

Average, Maximum and Minimum inductor currents

$$(2.3) \quad I_L = \frac{V_d D}{R(1-D)^2}$$

$$(2.4) \quad I_{\max} = I_L + \frac{V_d D}{2Lf}$$

$$(2.5) \quad I_{\min} = I_L - \frac{V_d D}{2Lf}$$

The boundary between CCM and DCM

$$(2.6) \quad (Lf)_{\min} = \frac{(1-D)^2 R}{2}$$

Minimum Inductance

$$(2.7) \quad L_{\min} = \frac{(1-D)^2 R}{2f}$$

Output Voltage Ripple

$$(2.8) \quad \frac{\Delta V_o}{V_o} = \frac{D}{RCf}$$

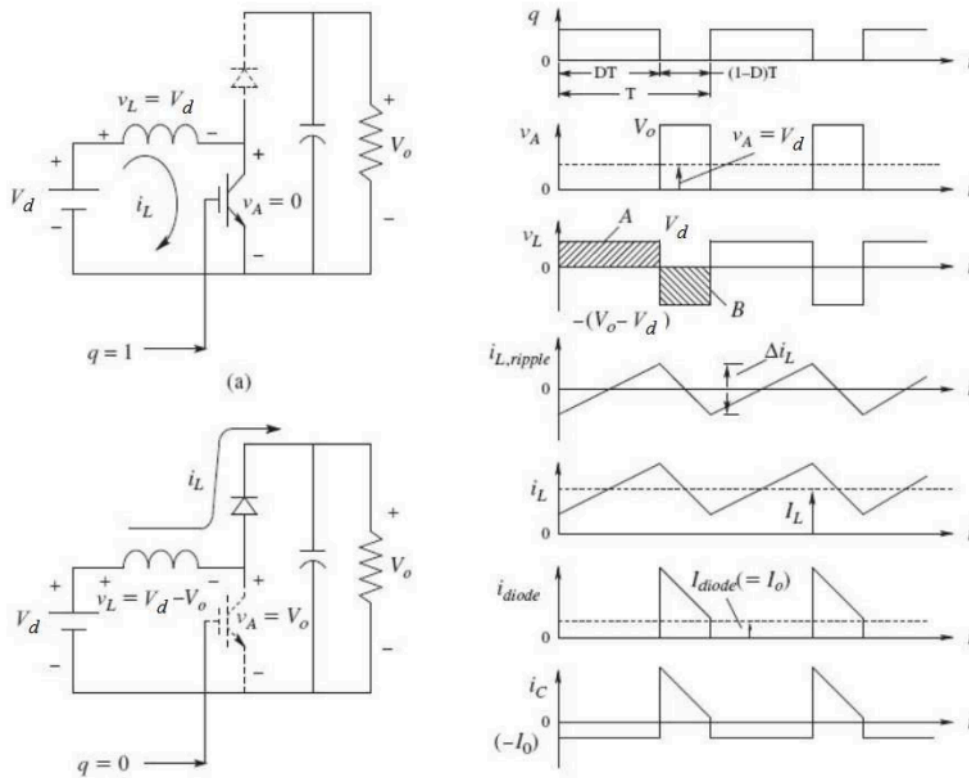


Figure 2.2 Waveforms of the buck-boost converter where the transistor acts as an ideal switch when **a)** closed, **b)** open. Note that the ground node here is where the positive output node in **Figure 2.1** is.

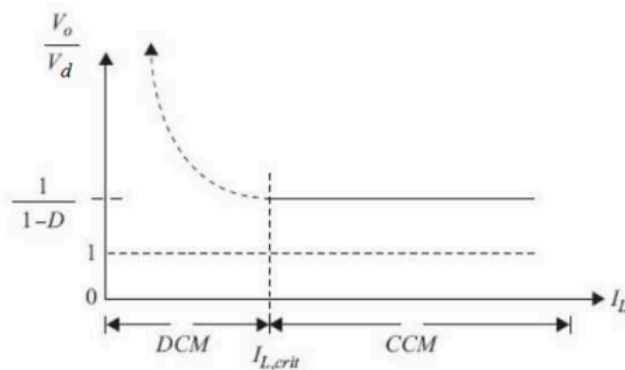


Figure 2.3 Voltage transfer ratio for the Buck-Boost converter with fixed D

Note that a combination of a switch and a diode is called a power-pole which can be represented as an ideal transformer with the turn ratio corresponding to Duty Cycle

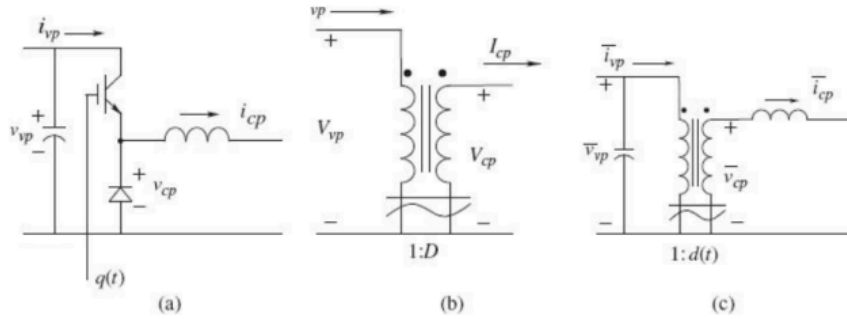


Figure 2.4 Dynamic averaging with an ideal transformer in CCM mode: **a)** switching model; **b)** an ideal transformer equivalent of the switch combination, aka “power-pole”, when operating in CCM; **c)** dynamic average modeling for small variations in operating parameters, aka “small-signal” analysis.

Voltage and Current ports

$$(2.9) \quad \begin{aligned} V_{cp} &= DV_{vp} \\ I_{vp} &= DI_{cp} \end{aligned}$$

Assuming further that all variables (V_{vp} , V_{cp} , I_{vp} , I_{cp} , D) vary slowly with respect to the switching frequency

$$(2.10) \quad \begin{aligned} V_{cp}(t) &= \bar{v}_{cp}(t), & V_{vp}(t) &= \bar{v}_{vp}(t) \\ I_{cp}(t) &= \bar{i}_{cp}(t), & I_{vp}(t) &= \bar{i}_{vp}(t) \\ D(t) &= d(t) \end{aligned}$$

Therefore (2.9) can be written as (2.11):

$$(2.11) \quad \begin{aligned} \bar{v}_{cp}(t) &= d(t) \bar{v}_{vp}(t) \\ \bar{i}_{vp}(t) &= d(t) \bar{i}_{cp}(t) \end{aligned}$$

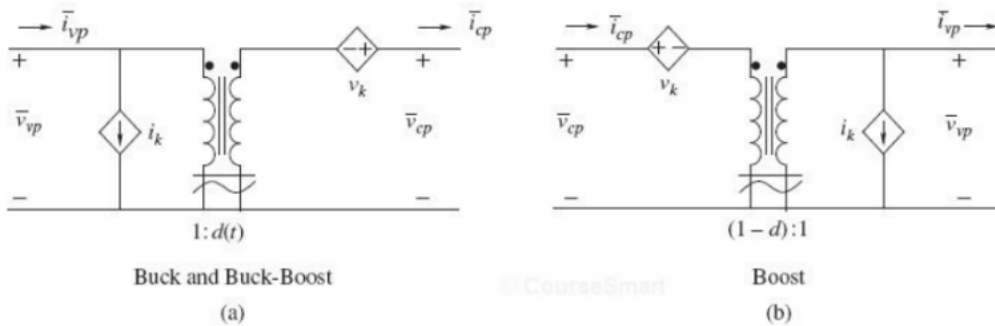


TABLE 2.1 v_k and i_k in DCM

Converter	v_k	i_k
Buck	$\left(1 - \frac{2Lf\bar{i}_L}{(V_d - \bar{v}_o)d}\right)\bar{v}_o$	$\frac{d^2}{2Lf} (V_d - \bar{v}_o) - d\bar{i}_L$
Boost	$\left(1 - \frac{2Lf\bar{i}_L}{V_d d}\right)(V_d - \bar{v}_o)$	$\frac{d^2}{2Lf} V_d - d\bar{i}_L$
Buck-Boost	$\left(1 - \frac{2Lf\bar{i}_L}{V_d d}\right)\bar{v}_o$	$\frac{d^2}{2Lf} V_d - d\bar{i}_L$

Note that v_k and i_k are zero in CCM and The DCM condition can be determined during run-time by checking the value of the inductor current i_L .

PART 3:

Because switching operations are non-linear, analyzing these are highly complicated. By linearizing switching functions using ideal CCM/DCM transformers. This allows for simpler analysis since it ignores small waveform ripples that are not essential during design. It allows the development of robust regulators using well-established system control methods. It is critical to understand the importance of system control analysis.

Prelab:

2. For the buck converter in Part 1, determine theoretically the critical load resistance value R_{Lcrit} at which the mode of operation is at the boundary between CCM and DCM. Assume D , L_{min} , f to be known. Hint: use (1.5).

$$(1.5) \quad L_{min} = \frac{(1-D)R}{2f}$$

$$D = 0.75$$

$$f = 100 \text{ kHz}$$

$$L_{min} = 100 \text{ uH}$$

$$(1-D)R = L_{min} \cdot 2f$$

$$R = L_{min} \cdot 2f / (1-D) = 80 \Omega$$

3. Derive inductor current ripple Δi_L for the buck converter in CCM mode from (1.2), (1.3).

$$(1.2) \quad I_{max} = V_o \left(\frac{1}{R} + \frac{1-D}{2Lf} \right)$$

$$(1.3) \quad I_{min} = V_o \left(\frac{1}{R} - \frac{1-D}{2Lf} \right)$$

$$(1.6) \quad L = \frac{V_o (1-D)}{\Delta i_L f}$$

$$I_{\max} = V_o ((1/R) + ((1-D)/(2Lf))) \Rightarrow R = ((2fLV_o) / (2fI_{\max}L + DV_o - V_o))$$

Plug in R into I_{\min}

$$I_{\min} = V_o ((1/R) - ((1-D)/(2Lf))) = V_o ((1/((2fLV_o) / (2fI_{\max}L + DV_o - V_o))) - ((1-D)/(2Lf)))$$

$$I_{\min} = (fLI_{\max} - DV_o + V_o) / fL = I_{\min} - I_{\max} = (V_o(1-D)) / (fL)$$

$$\Rightarrow \Delta i_L = (V_o/L) * ((1-D)/f)$$

4. Derive inductor current ripple Δi_L for the buck-boost converter in CCM mode from (2.4), (2.5).

$$(2.3) \quad I_L = \frac{V_d D}{R(1-D)^2}$$

$$(2.4) \quad I_{\max} = I_L + \frac{V_d D}{2Lf}$$

$$(2.5) \quad I_{\min} = I_L - \frac{V_d D}{2Lf}$$

$$I_{\max} = I_L + ((V_d D)/(2Lf)) \Rightarrow I_L = ((2fI_{\max}L - DV_d) / (2fL))$$

Plug I_L into I_{\min}

$$I_{\min} = I_{\max} = I_L + ((V_d D)/(2Lf)) = ((2fI_{\max}L - DV_d) / (2fL)) + ((V_d D)/(2Lf)) = (fI_{\max}L - DV_d) / (fL)$$


$$I_{\min} - I_{\max} = (-DV_d) / (fL)$$

$$= \Delta i_L = (V_d D)/(fL)$$


Design Calculations and Circuit Schematic, including Experimental Data and Data Analysis:

1.2:


1)

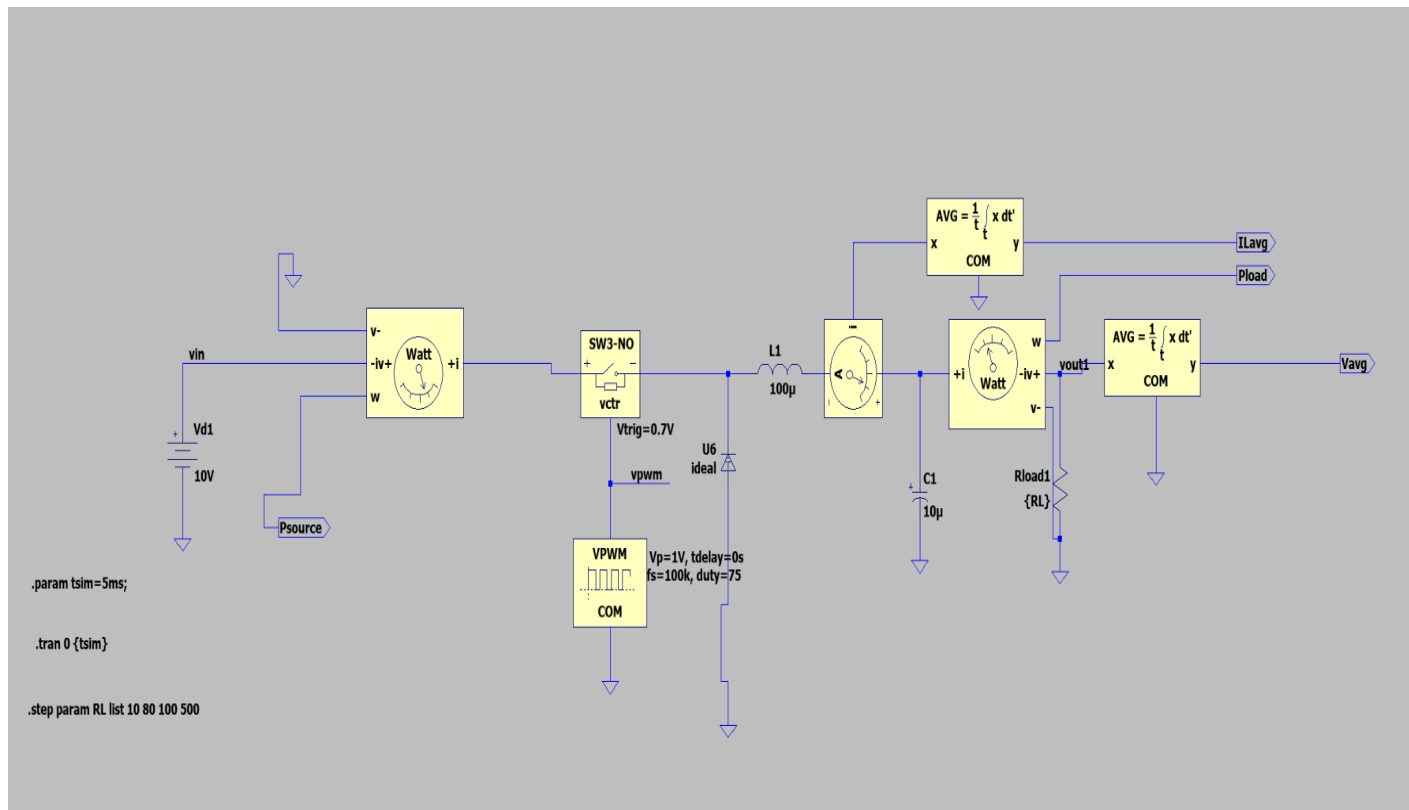

3)

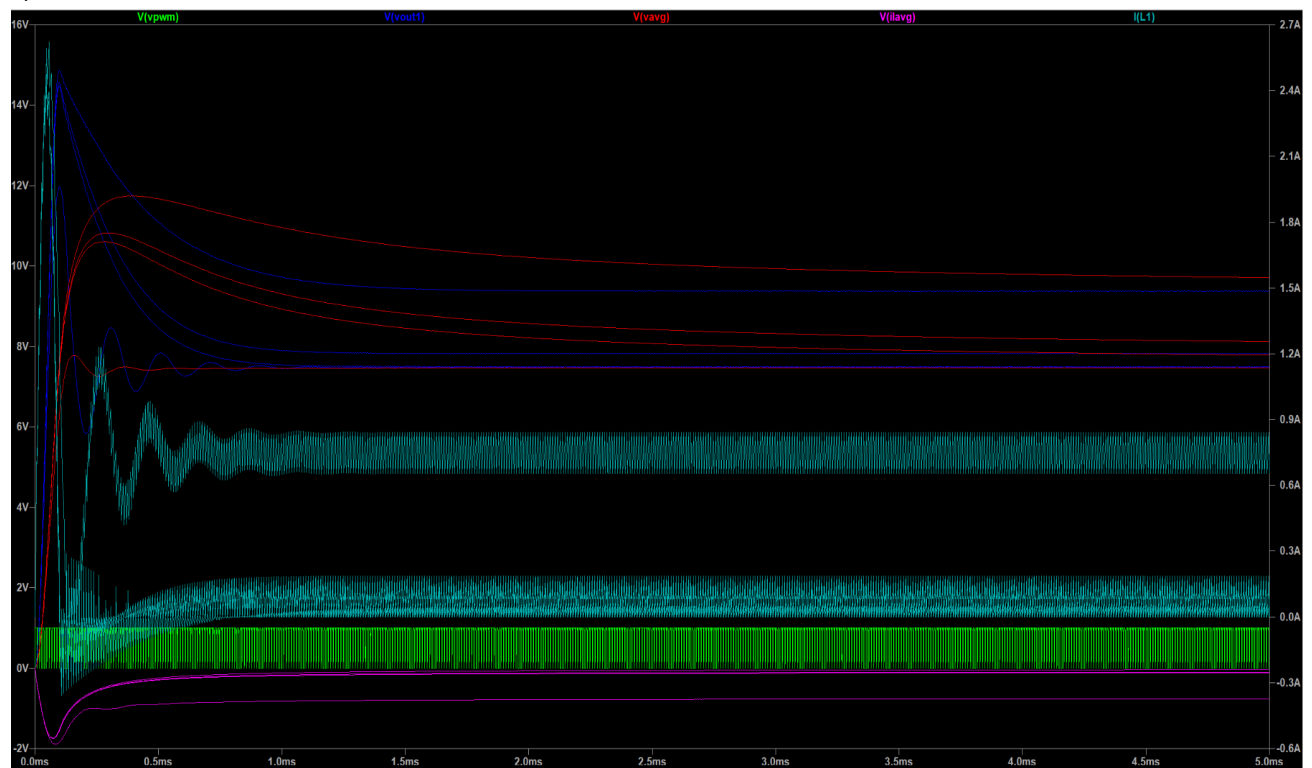


Vpwm

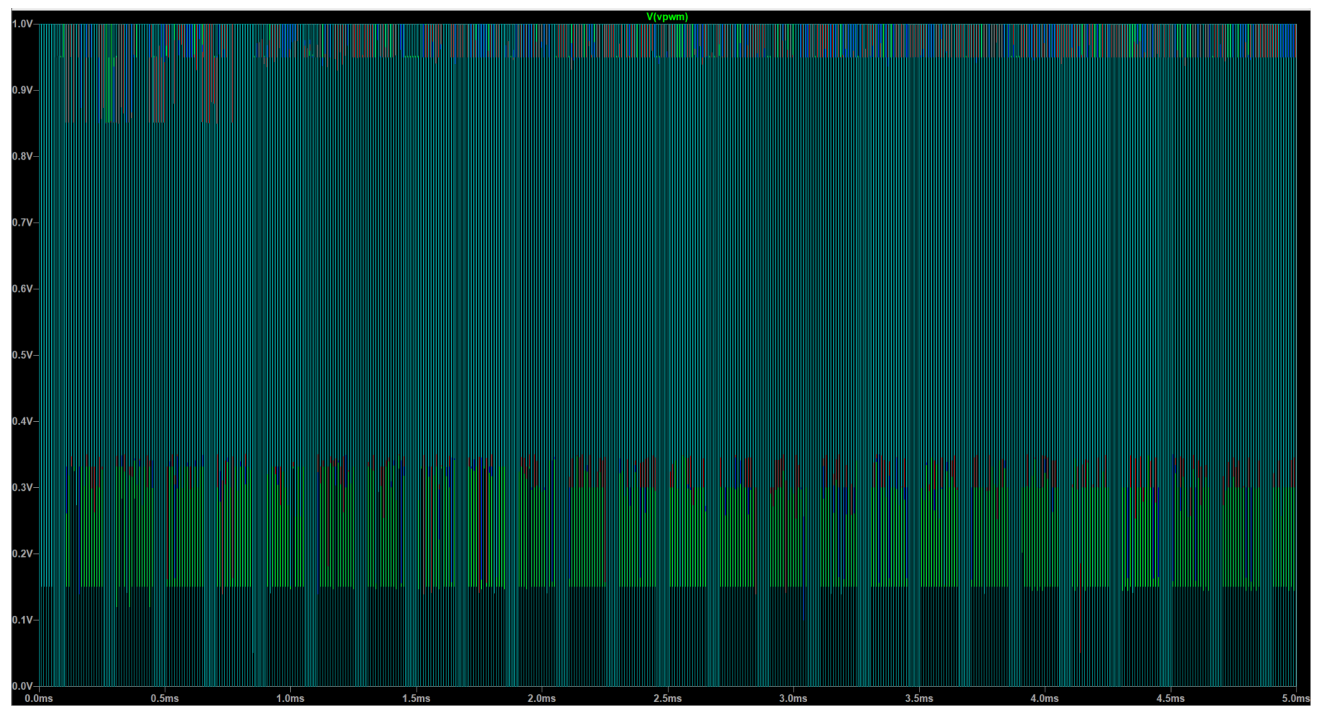


Vout




Vavg

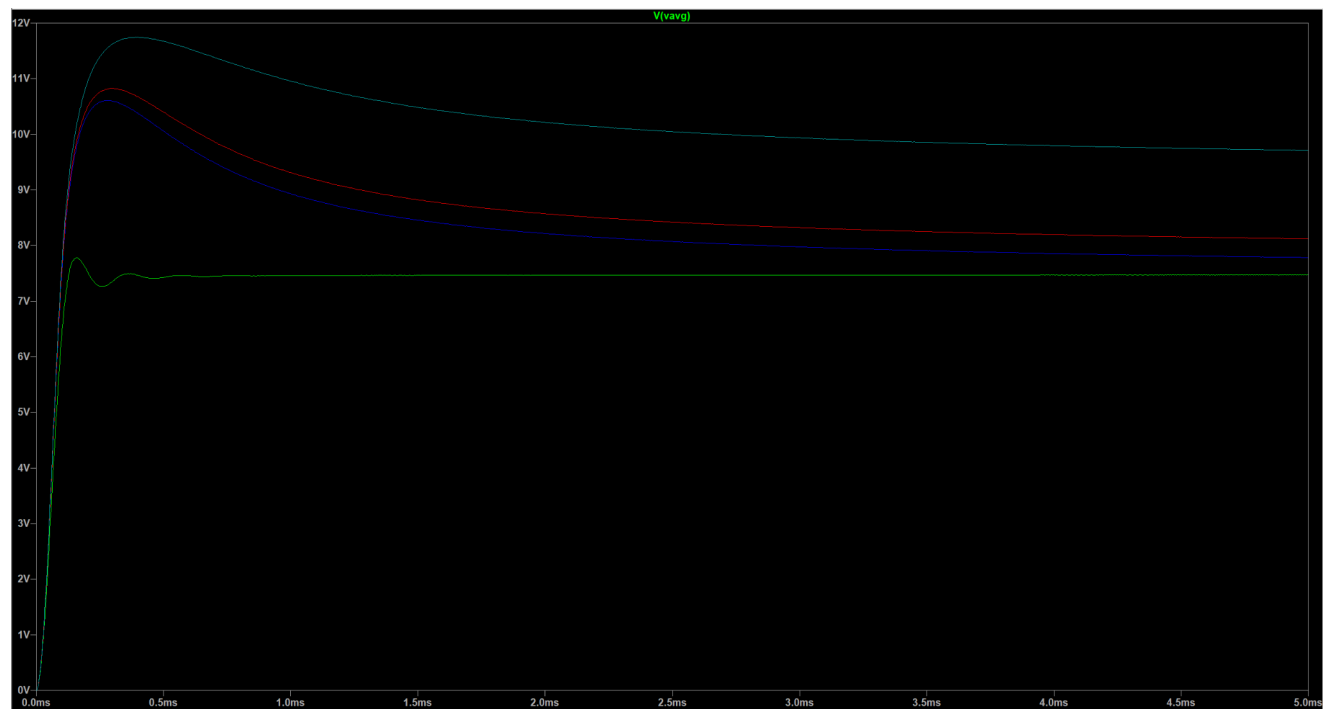

Vilavg

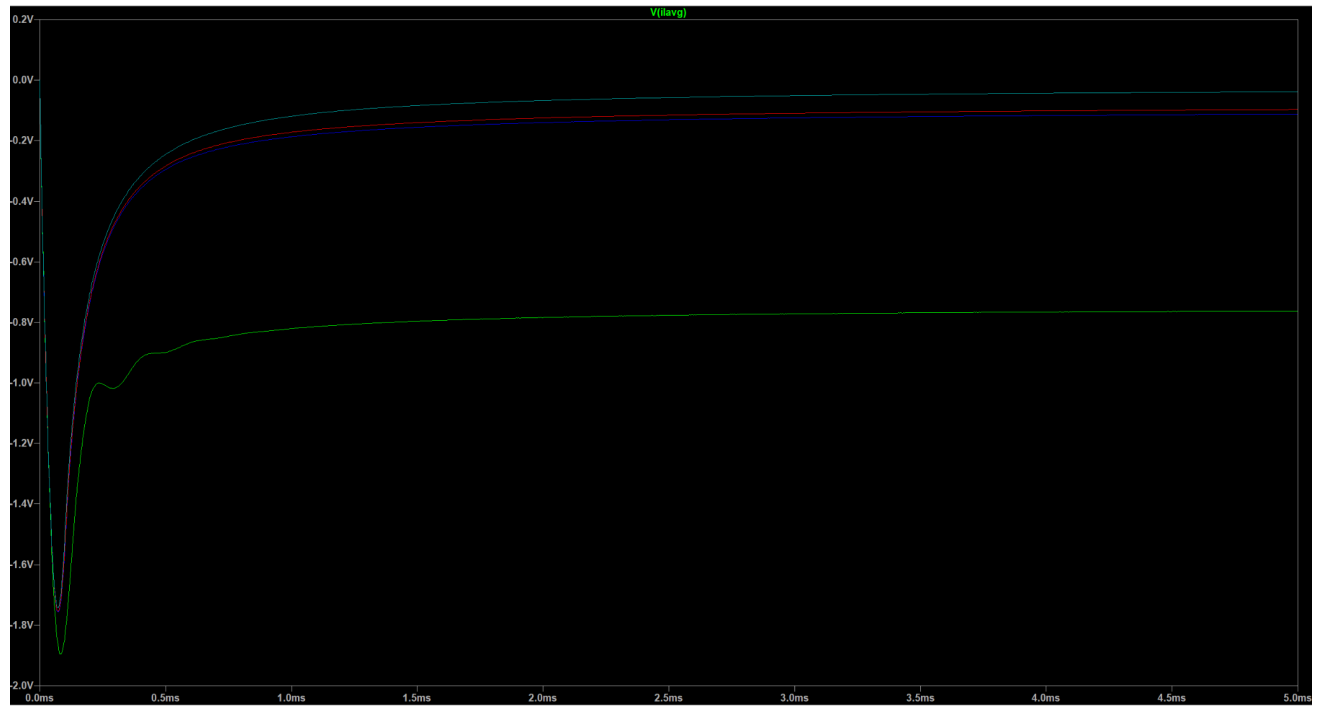

llavg

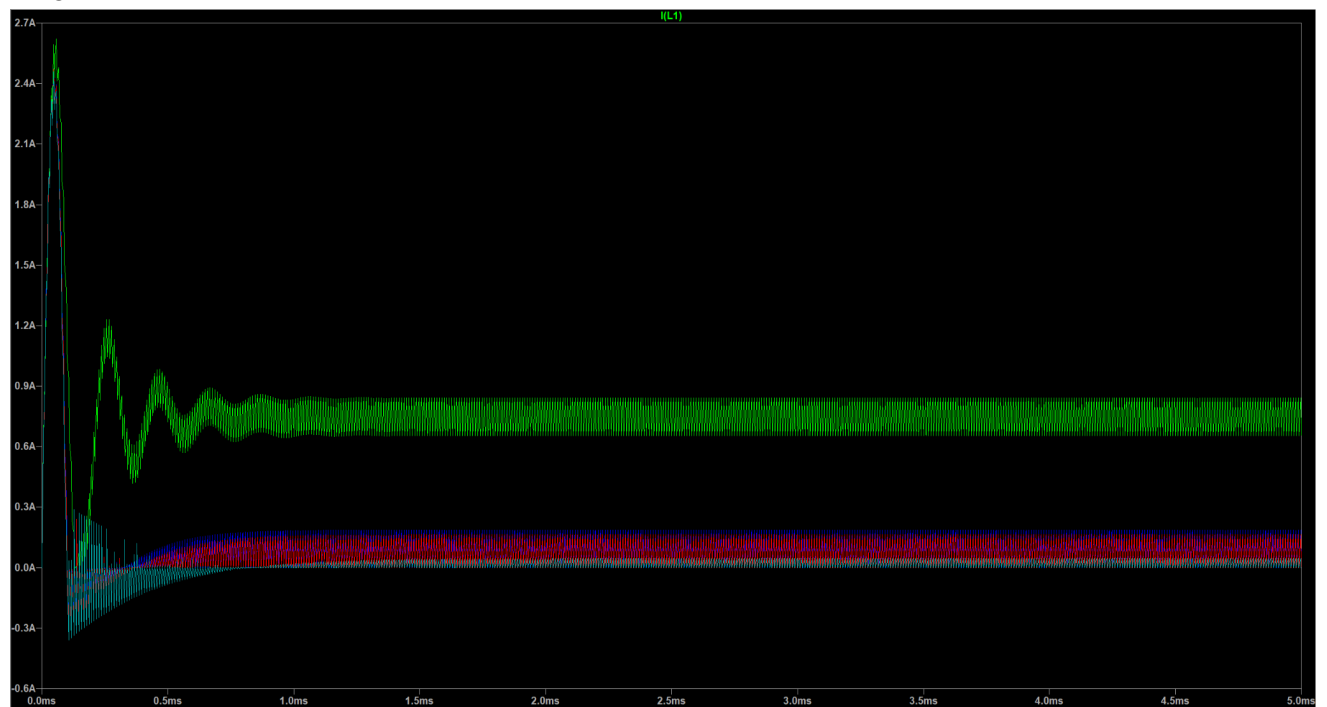

4)

$$D = 0.75$$


$$f = 100 \text{ kHz}$$

$$L_{\min} = 100 \text{ }\mu\text{H}$$


$$R_{L, \text{CRIT}} = L_{\min} \cdot 2f / (1-D) = 80 \text{ }\Omega$$

Here we can see that we calculated $R_{L, \text{Crit}}$ using Eq(1.5) which is the lowest possible value for L


6)

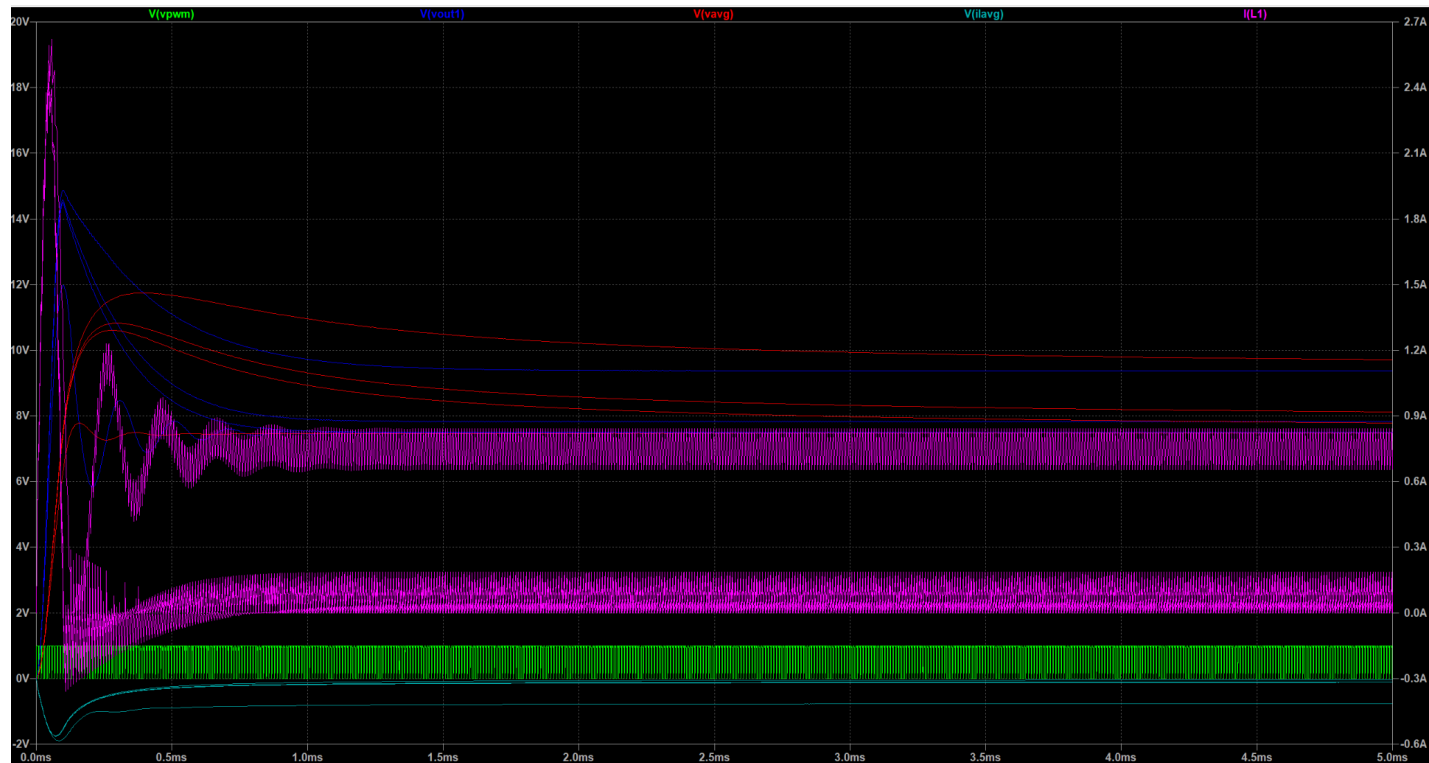


Vpwm

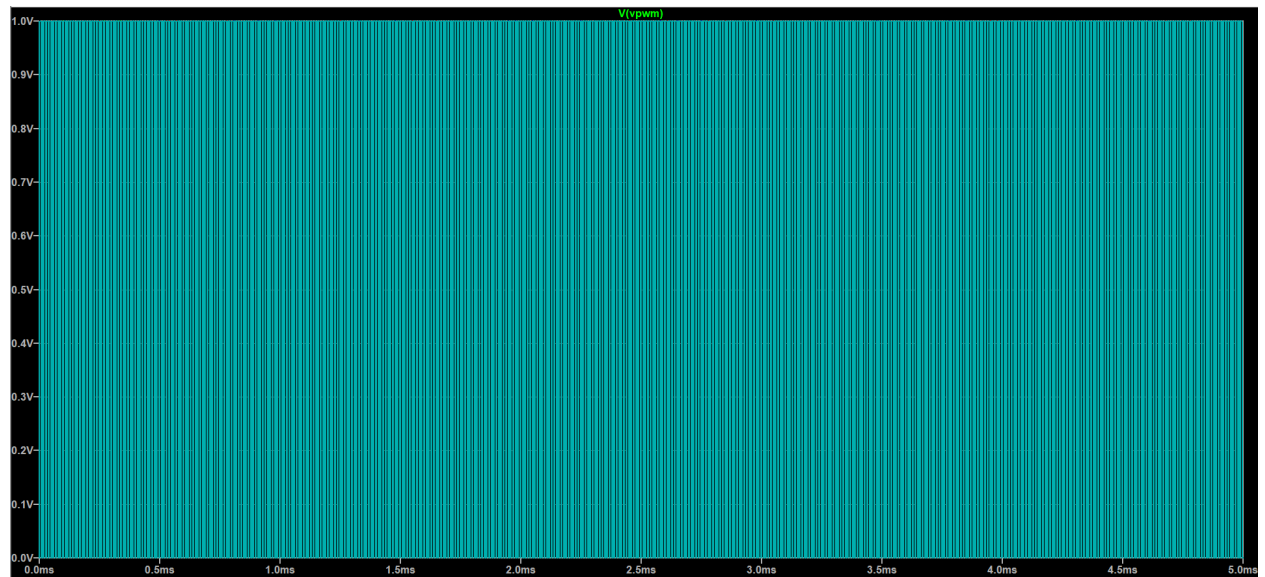


Vout, Vavg

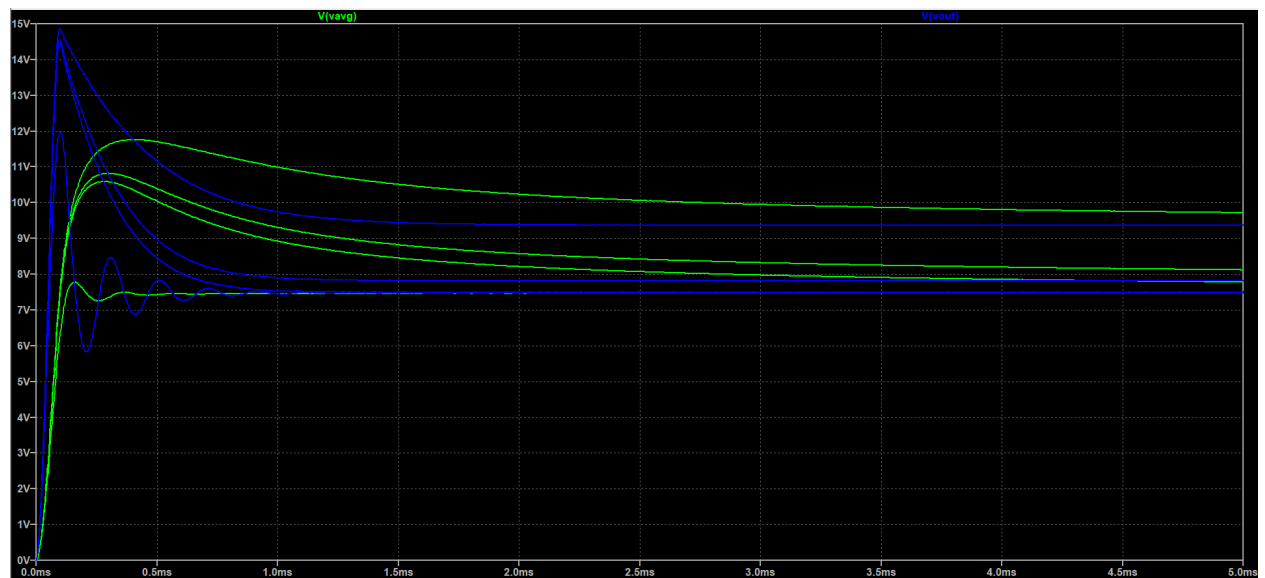

L1, ILavg

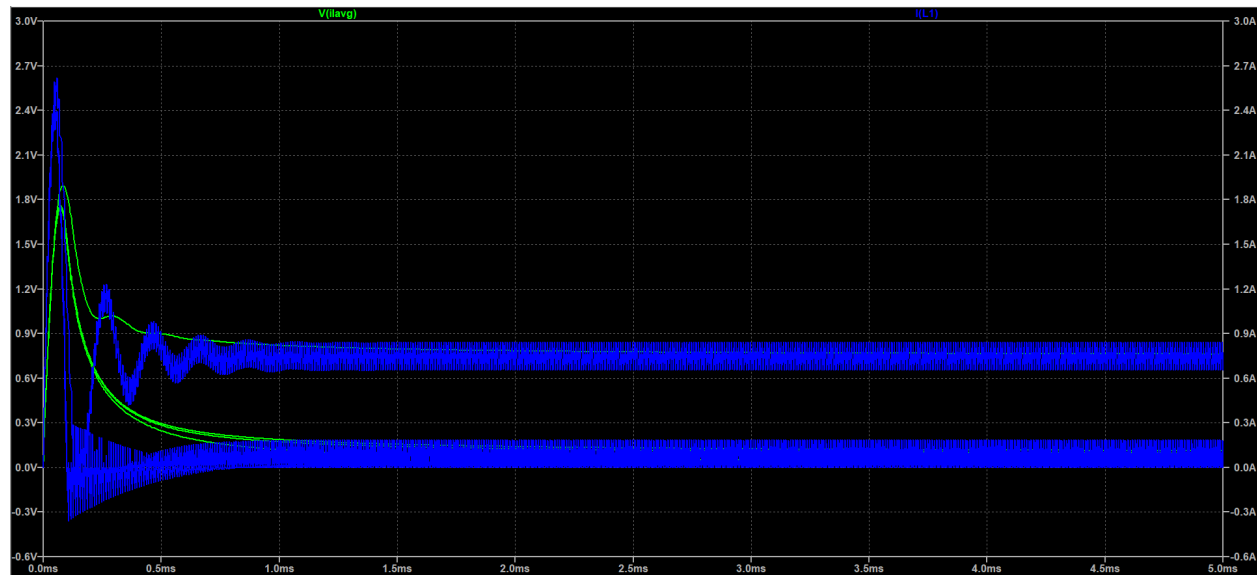


VPsource, VPload

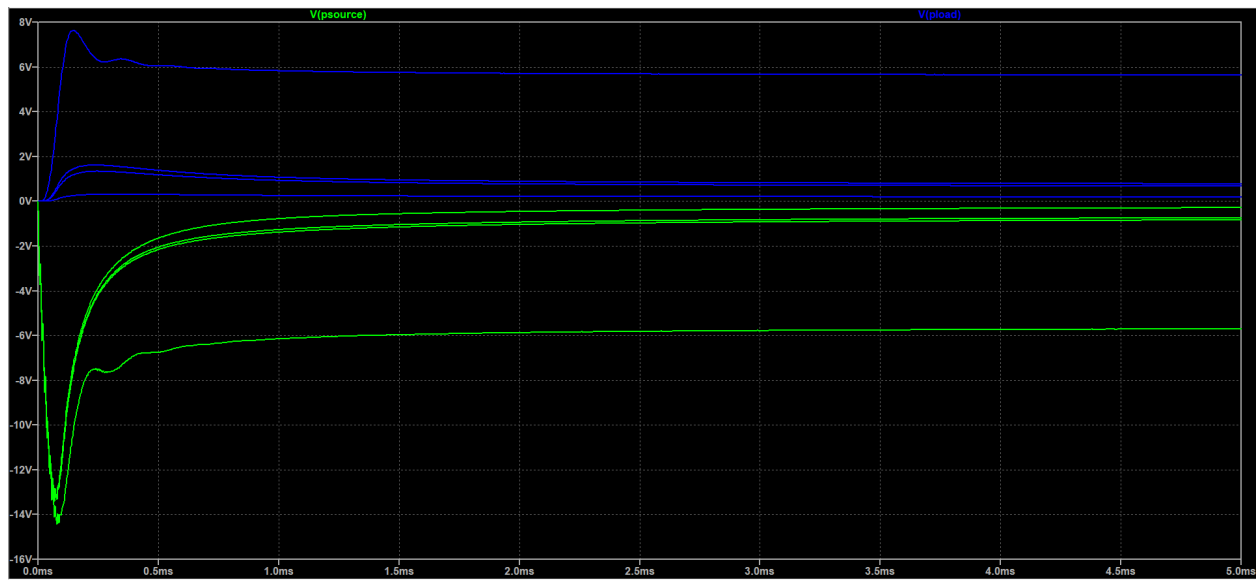

8)

Experimental

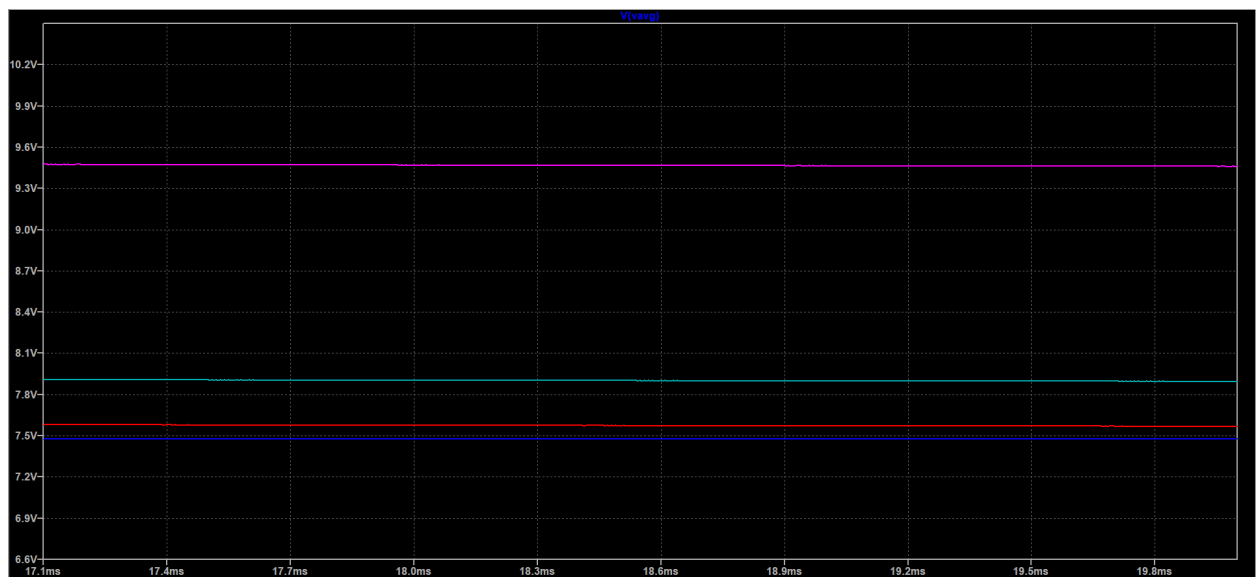

At $R_L = 10 \Omega$, $V_o = 7.47 \text{ V}$

At $R_L = 80 \Omega$, $V_o = 7.57 \text{ V}$

At $R_L = 100 \Omega$, $V_o = 7.89 \text{ V}$

At $R_L = 500 \Omega$, $V_o = 9.46 \text{ V}$

Theoretical

$$(1.1) \quad V_o = DV_d$$

$$(1.9) \quad V_o = V_d \frac{2D}{D + \sqrt{D^2 + 8 \frac{Lf}{R}}}$$

At $R_L = 10 \, \Omega$ (CCM)

$$V_o = DV_d = 0.75 \cdot 10V = 7.5 \, V$$

At $R_L = 80 \, \Omega$ (edge of CCM and DCM)

$$V_o = DV_d = 0.75 \cdot 10V = 7.5 \, V$$

$$V_o = V_d \left(\frac{2D}{D + \sqrt{D^2 + (8Lf/R)}} \right) \\ = 10 \cdot \left(\frac{2 \cdot 0.75}{0.75 + \sqrt{0.75^2 + ((8 \cdot 100 \cdot 10^{-6} \cdot 100 \cdot 10^3)/80)}} \right) = 7.5 \, V$$

At $R_L = 100 \, \Omega$ (DCM)

$$V_o = V_d \left(\frac{2D}{D + \sqrt{D^2 + (8Lf/R)}} \right) \\ = 10 \cdot \left(\frac{2 \cdot 0.75}{0.75 + \sqrt{0.75^2 + ((8 \cdot 100 \cdot 10^{-6} \cdot 100 \cdot 10^3)/80)}} \right) = 7.82 \, V$$


At $R_L = 500 \, \Omega$ (DCM)

$$V_o = V_d \left(\frac{2D}{D + \sqrt{D^2 + (8Lf/R)}} \right) \\ = 10 \cdot \left(\frac{2 \cdot 0.75}{0.75 + \sqrt{0.75^2 + ((8 \cdot 100 \cdot 10^{-6} \cdot 100 \cdot 10^3)/80)}} \right) = 9.375 \, V$$

9)


Experimental

$R_L = 10 \, \Omega$

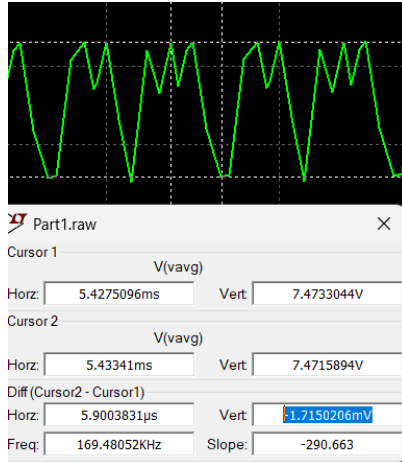

$$\Delta V_o / V_o = 1.72 \, mV$$

$R_L = 80 \, \Omega$

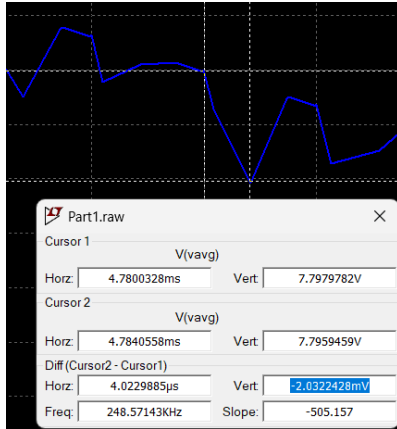

$$\Delta V_o / V_o = 2.03 \text{ mV}$$

Theoretical

$$(1.7) \quad \frac{\Delta V_o}{V_o} = \frac{1-D}{8LCf^2}$$


Note: at CCM all $V_o = 7.5 \text{ V}$

$$\Delta V_o / V_o = (V_o)(1-D)/(8LCf^2) = (1-0.75) / (8 \cdot 100 \cdot 10^{-6} \cdot 10 \cdot 10^{-6} \cdot (100 \cdot 10^3)^2) = 0.003125 \text{ V} = 3.13 \text{ mV}$$

10)


Experimental

$$R_L = 10 \Omega$$

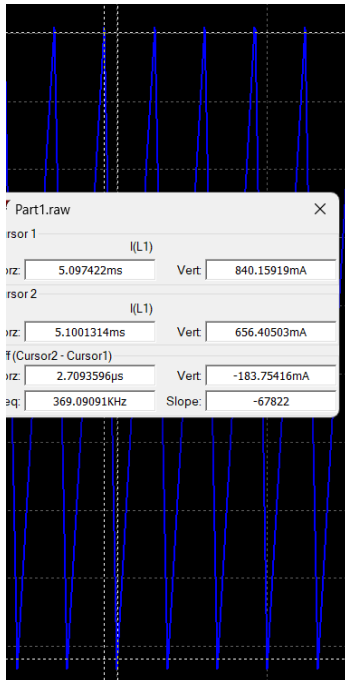

$$\Delta i_L = 183.75 \text{ mA}$$

$$R_L = 80 \Omega$$

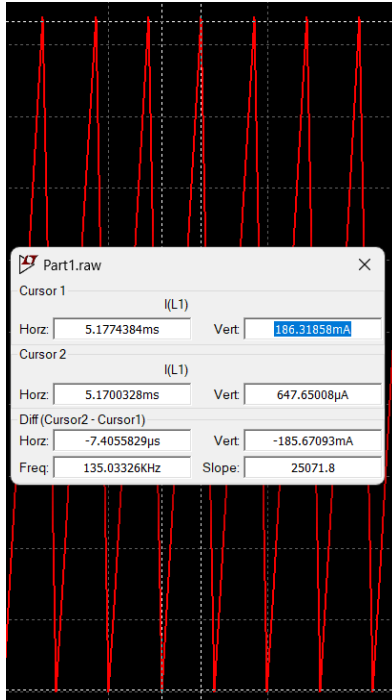

$$\Delta i_L = 185.67 \text{ mA}$$

Theoretical


Δi_L is Independent of R in CCM

$$\Delta i_L = (V_o/L) * ((1-D)/f) = (7.5/(100*10^{-6})) * ((1-0.75) / (100*10^3)) = 0.1875 = 187.5 \text{ mA}$$


Here we can see that both values are very similar to one another

11)

Experimental

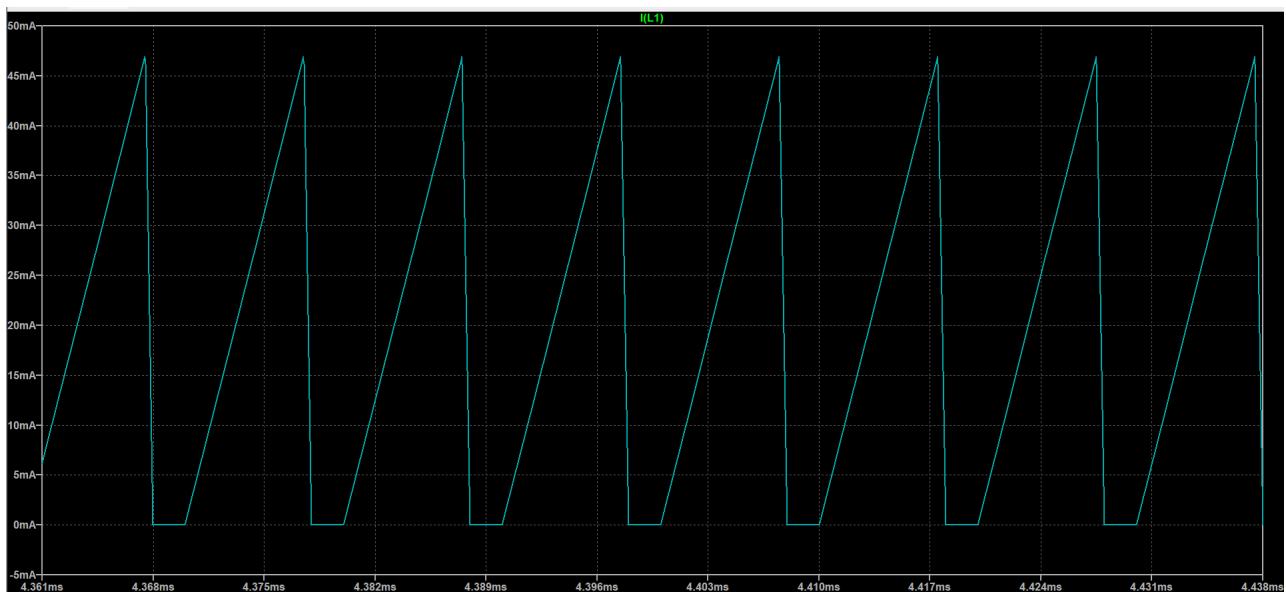


Positive Slope

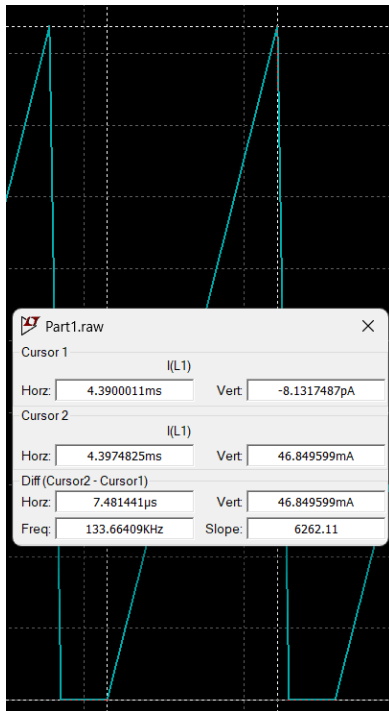

$$\text{Slope} = 46.85 \text{ mA} / 7.48 \text{ us} = 6263.37$$

Negative Slope

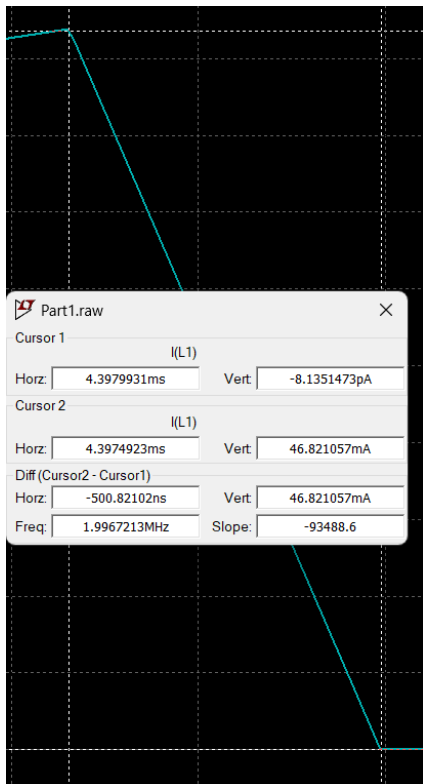

$$\text{Slope} = 46.82 \text{ mA} / 500.82 \text{ ns} = -93488.68$$

Theoretical:

Positive Slope

$$\text{Slope} = (V_d - V_o) / L_1 = (10 - 7.5) / (100 \cdot 10^{-6}) = 25000$$

Negative Slope

$$\text{Slope} = -V_o / L_1 = -7.5 / (100 \cdot 10^{-6}) = -75000$$

Here we can see that the slope values are very different but also it is important to note that they are all equally very large. They seem to follow the same trend of the how the positive slope is always smaller than the negative slope. These differences could be due to the manual way of measuring resulting in big changes in the slope

12)

Experimental

At $R_L = 10 \Omega$ (CCM)

$$I_{\max} = 841.895 \text{ mA}$$

$$I_{\min} = 653.424 \text{ mA}$$

At $R_L = 80 \Omega$ (edge of CCM and DCM)

$$I_{\max} = 187.630 \text{ mA}$$

$$I_{\min} = 0 \text{ mA}$$

Theoretical

$$(1.2) \quad I_{\max} = V_o \left(\frac{1}{R} + \frac{1-D}{2Lf} \right)$$

$$(1.3) \quad I_{\min} = V_o \left(\frac{1}{R} - \frac{1-D}{2Lf} \right)$$

At $R_L = 10 \Omega$ (CCM)

$$I_{\max} = 7.5 \cdot \left((1/10) + ((1-0.75)/(2 \cdot 100 \cdot 10^{-6} \cdot 100 \cdot 10^{-3})) \right) = 0.84 \text{ A} = 840 \text{ mA}$$

$$I_{\min} = 7.5 \cdot \left((1/10) - ((1-0.75)/(2 \cdot 100 \cdot 10^{-6} \cdot 100 \cdot 10^{-3})) \right) = 0.66 \text{ A} = 660 \text{ mA}$$

At $R_L = 80 \Omega$ (edge of CCM and DCM)


$$I_{\max} = 7.5 \cdot \left((1/80) + ((1-0.75)/(2 \cdot 100 \cdot 10^{-6} \cdot 100 \cdot 10^{-3})) \right) = 0.19 \text{ A} = 190 \text{ mA}$$

$$I_{\min} = 7.5 \cdot \left((1/80) - ((1-0.75)/(2 \cdot 100 \cdot 10^{-6} \cdot 100 \cdot 10^{-3})) \right) = 0 \text{ A}$$

We can see that both values agree with each other

13)

I_{L1} , I_{Lavg} , V_{out} , V_{avg}

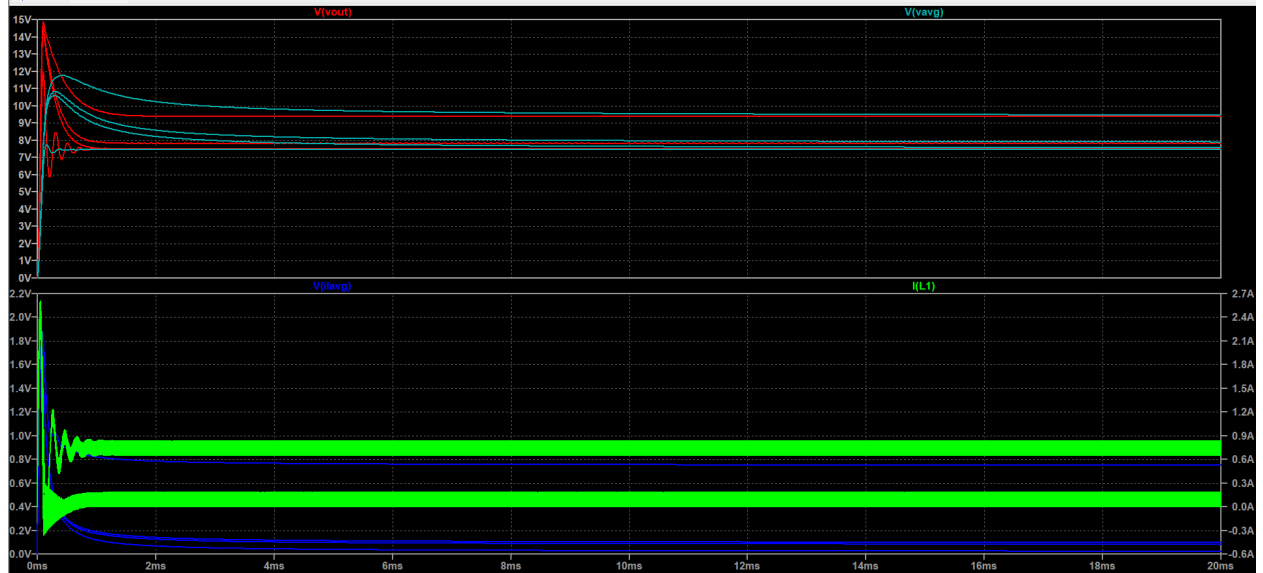

14)

$$(1.10) \quad \eta = \frac{\text{power consumed by the load}}{\text{power generated}} \times 100\% = \left| \frac{P_{out}}{P_{in}} \right| \times 100\%$$

At $R_L = 10 \, \Omega$ (CCM)

$$n = (5.62 \, \text{W} / 5.60 \, \text{W}) * 100 = 100.36\%$$

At $R_L = 80 \, \Omega$ (edge of CCM and DCM)

$$n = (721.60 \, \text{mW} / 737.64 \, \text{mW}) * 100 = 97.83\%$$

At $R_L = 100 \, \Omega$ (DCM)


$$n = (628.62 \, \text{mW} / 646.87 \, \text{mW}) * 100 = 97.18\%$$

At $R_L = 500 \, \Omega$ (DCM)

$$n = (179.92 \, \text{mW} / 205.09 \, \text{mW}) * 100 = 87.73\%$$


2.2

The schematic:

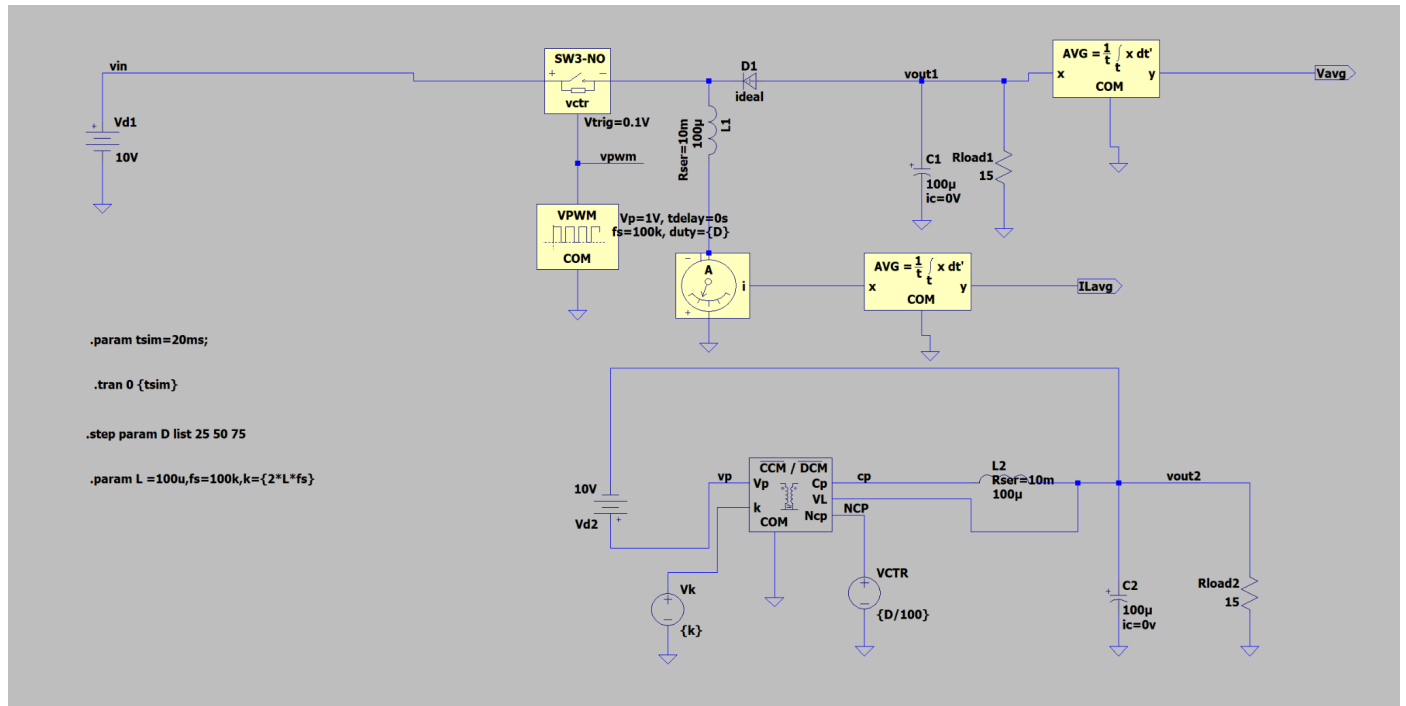


3)


D=0.25, D= 0.5, and D=0.75

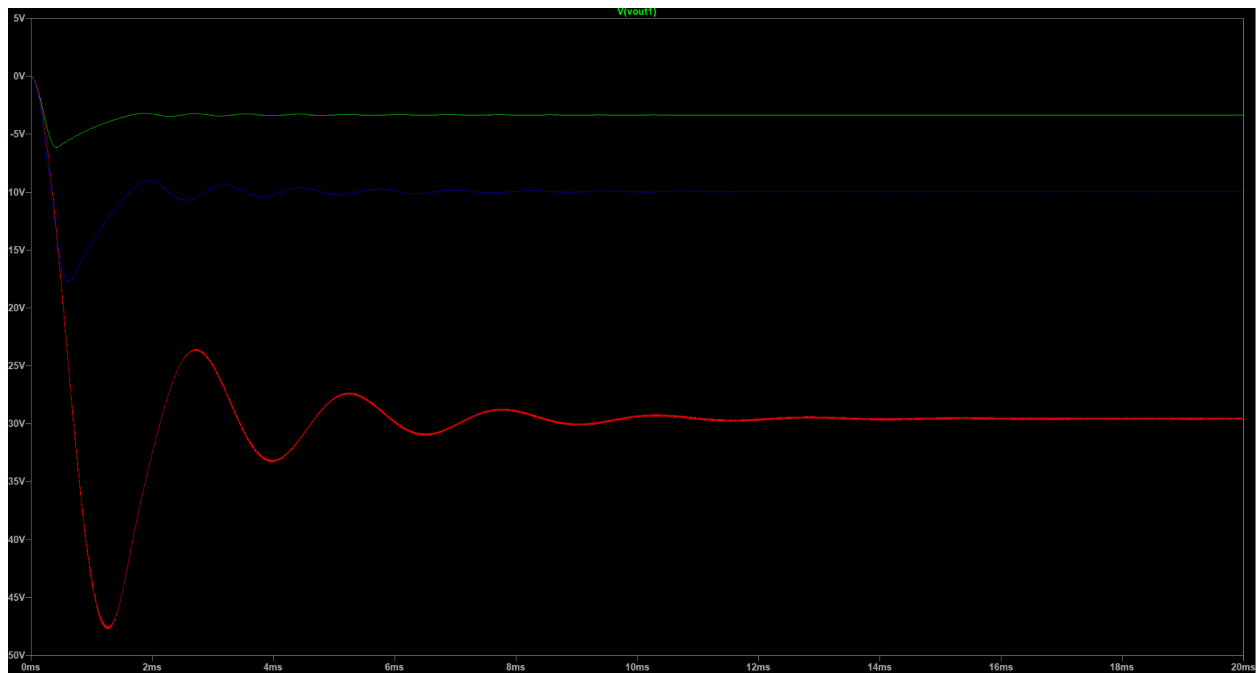


When step Duty cycle =25:

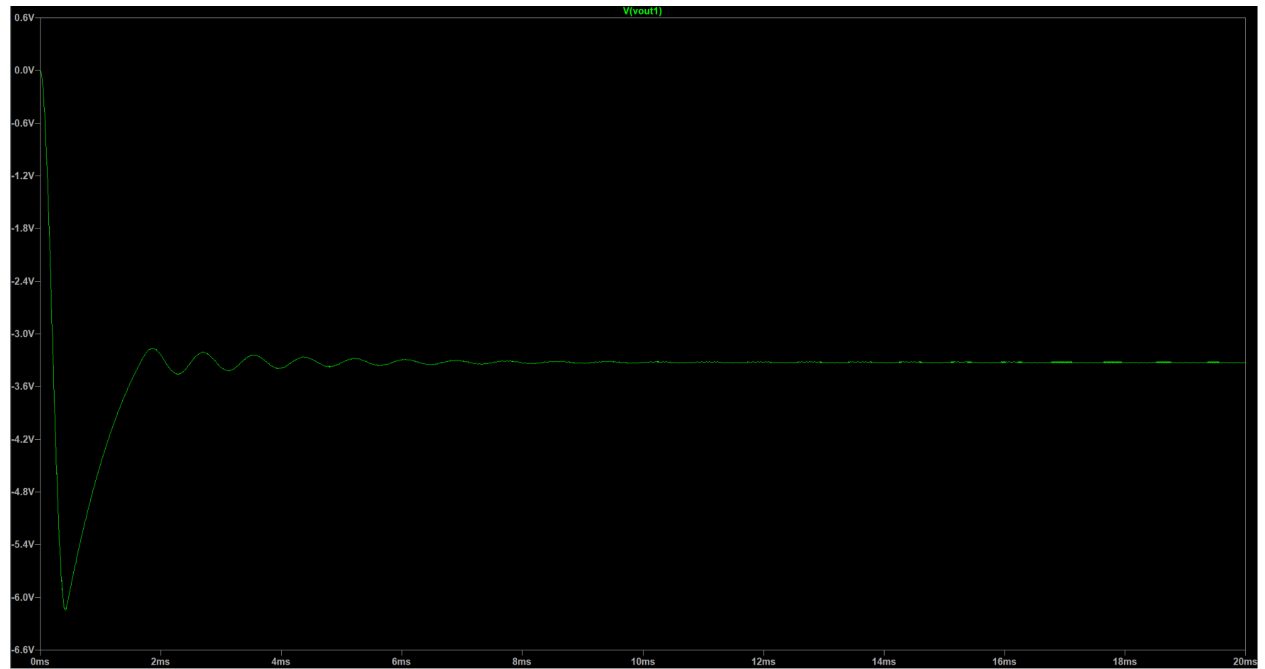


When step Duty Cycle =50:

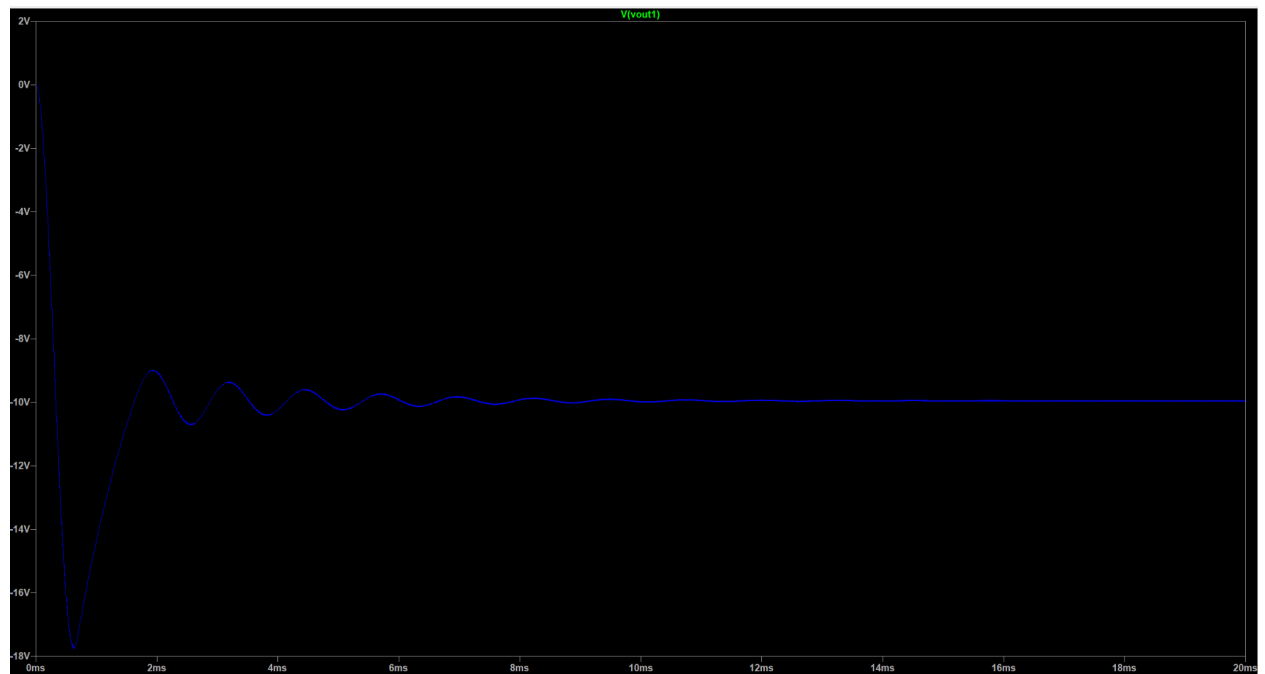


When step Duty Cycle = 75:

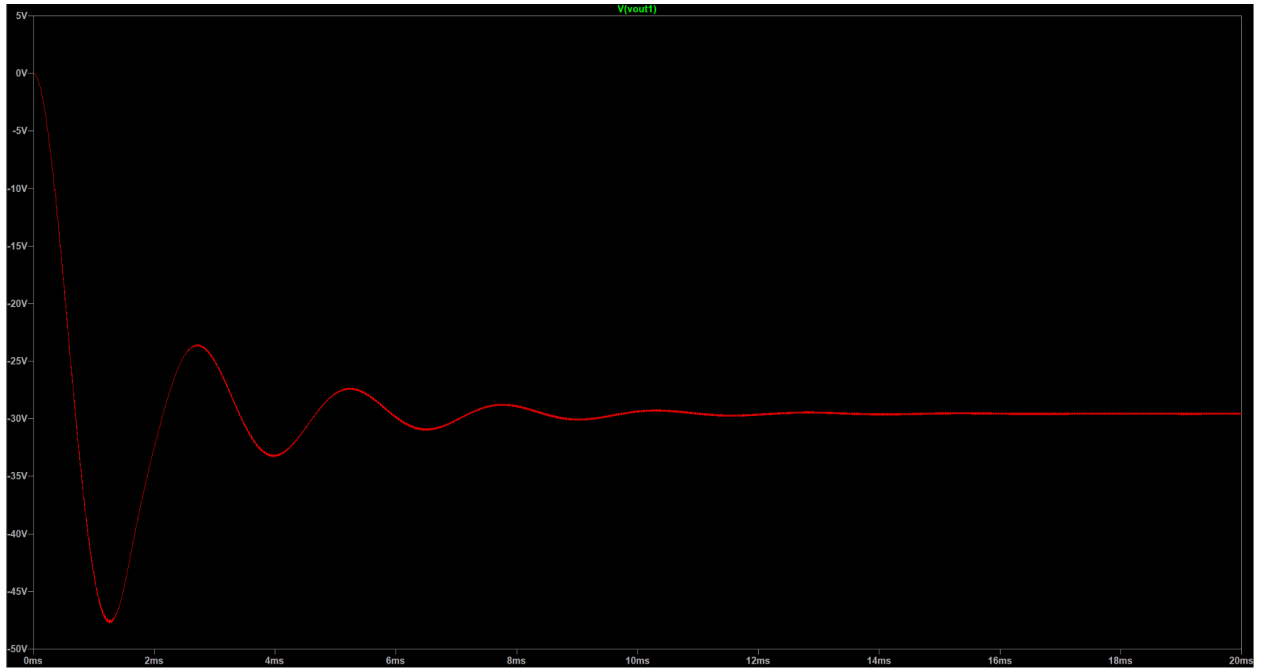


IL1, IL2, VOUT1

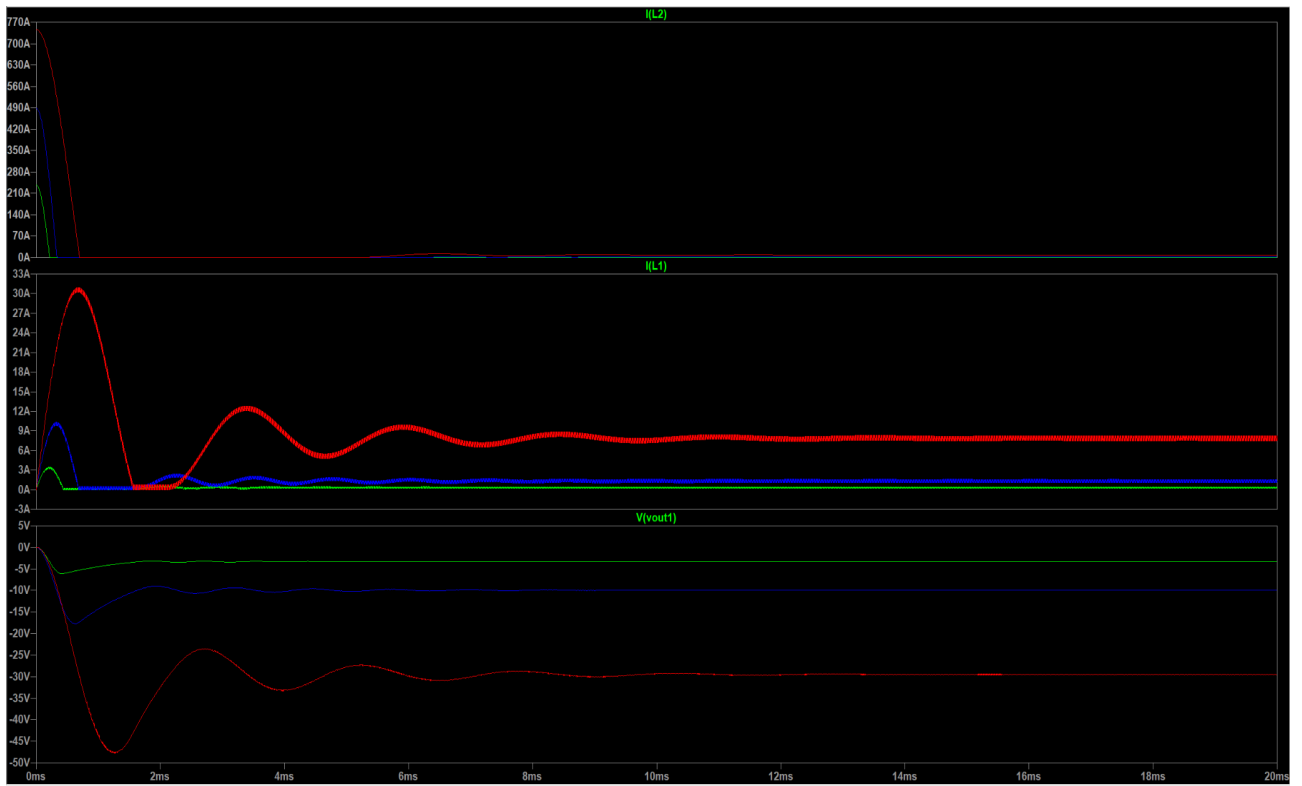

IL1

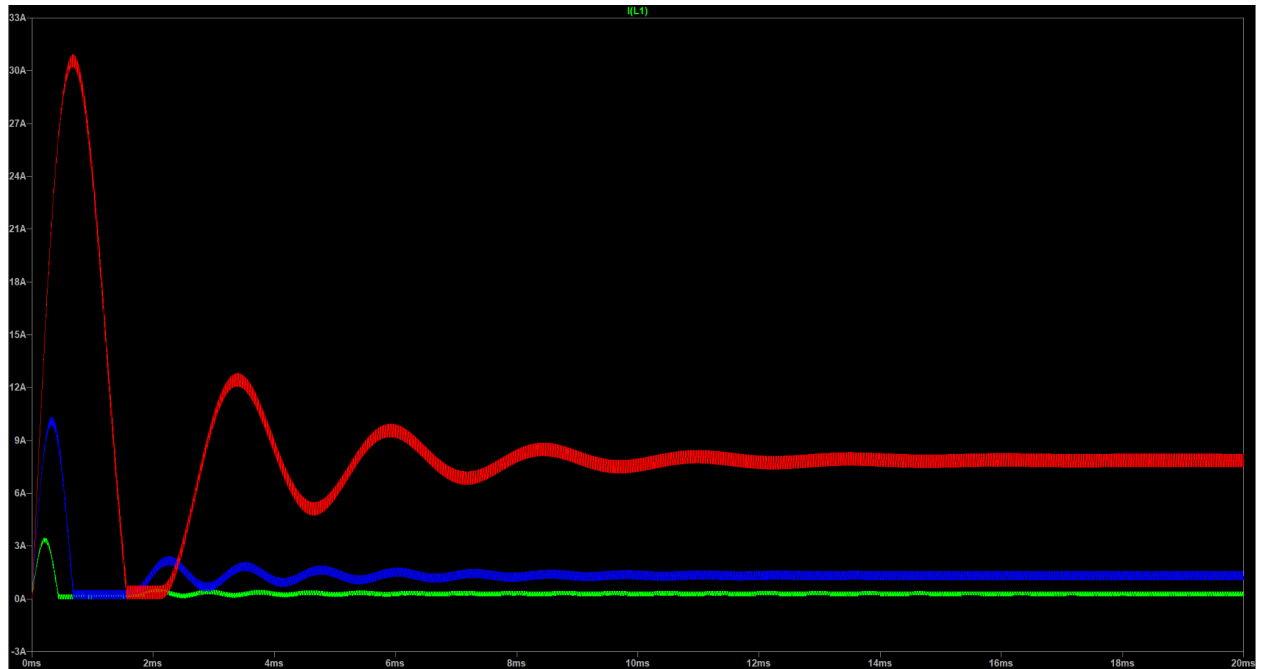

IL2:

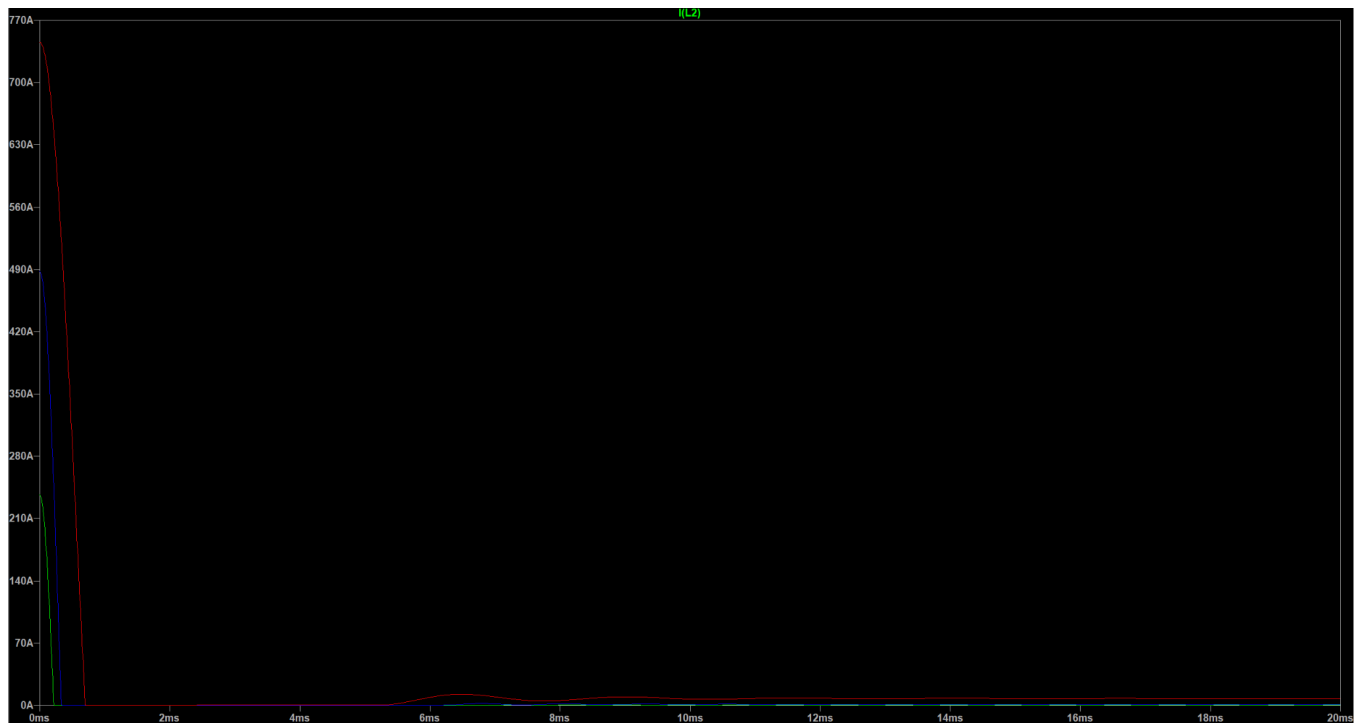


5)

if $D > 0.5$, the output voltage is greater than the input voltage (stepped-up), and if $D < 0.5$, the output voltage is less than the input voltage (stepped-down).

$$V_o = -V_d \frac{D}{1-D}$$

For step when D=25

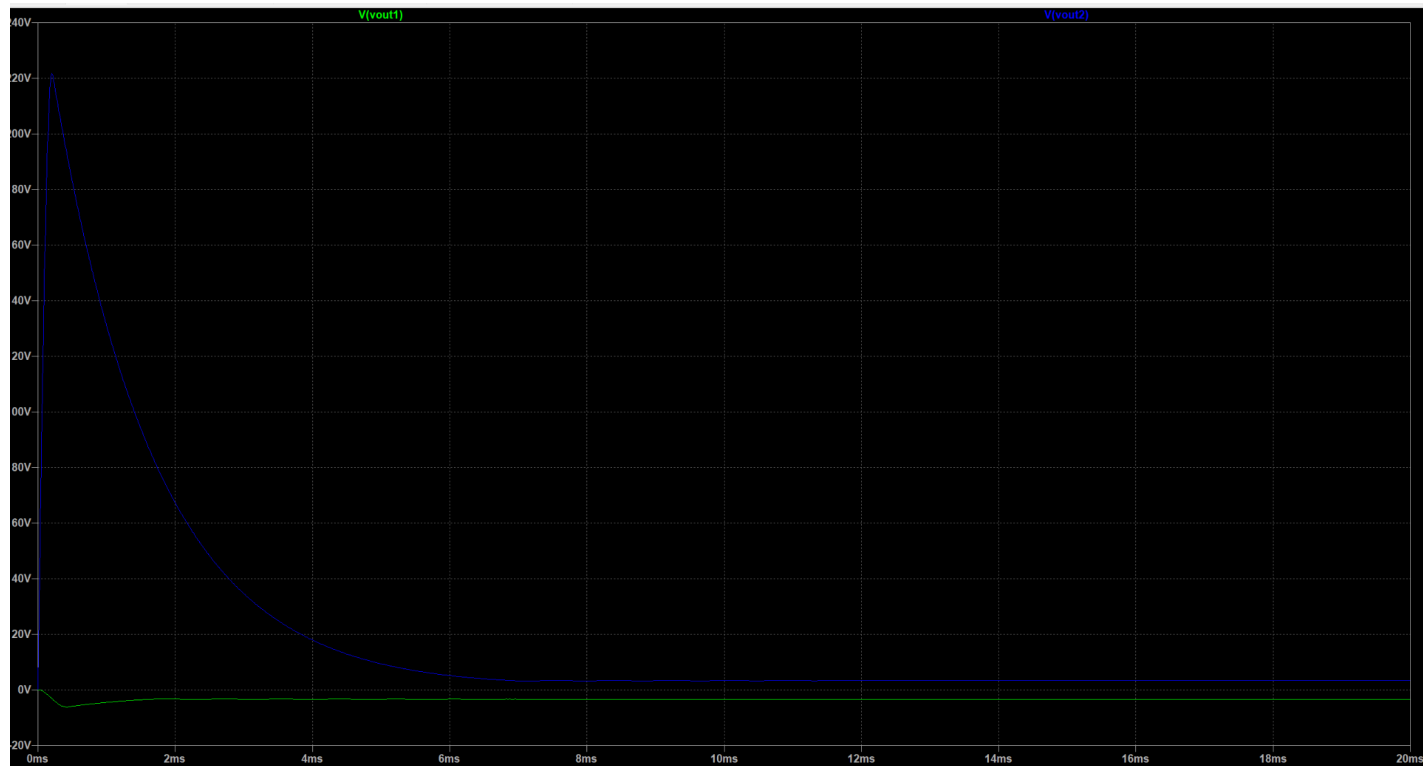

Vout1= -3V

Based on the experiment, Vout= -3 V, Vd=10V

$-3 = -10 \frac{D}{1-D}$ -> $D=0.23$ -> **Step down voltage**

Vout 2= 3.196

$3.196 = -10 \frac{D}{1-D}$ -> $D= -0.46$ -> **step down voltage**

For step when D=50




Vout1= -10V

Based on the experiment, $V_{out} = -10\text{ V}$, $V_d = 10\text{ V}$


$-10 = -10(D/1-D) \rightarrow D = 0.5 \rightarrow$ **Step up voltage**

Vout 2= 9.4V

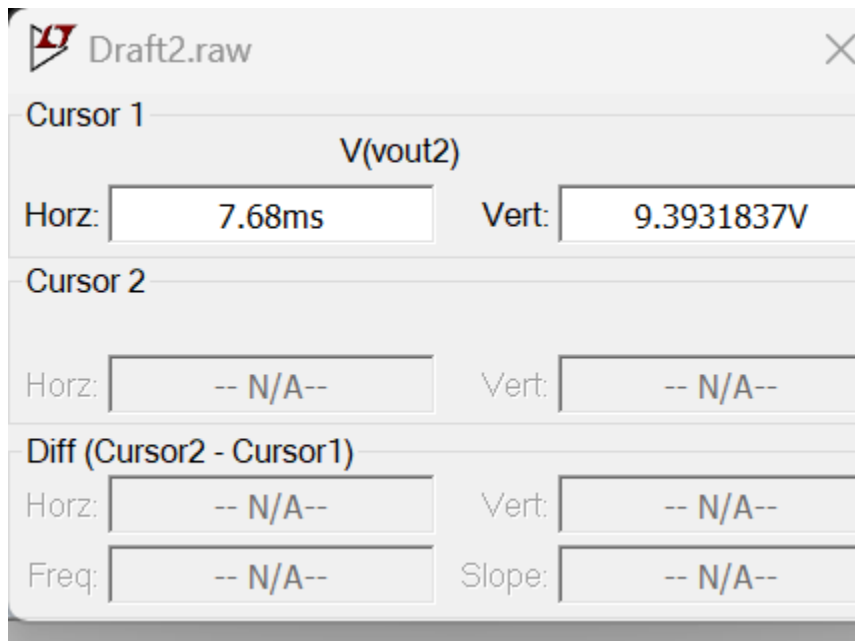


$9.2 = -10(D/1-D) \rightarrow D = -11.5 \rightarrow$ **step down voltage**

For step when D=75

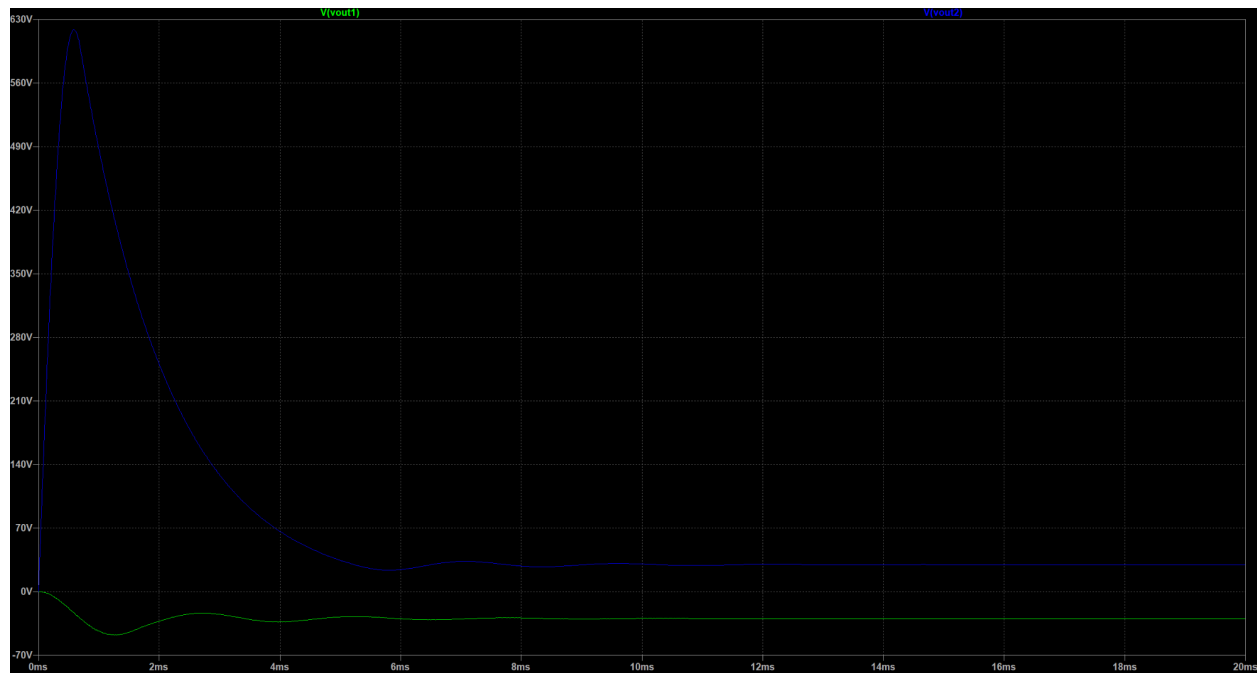


Vout1= -28.96

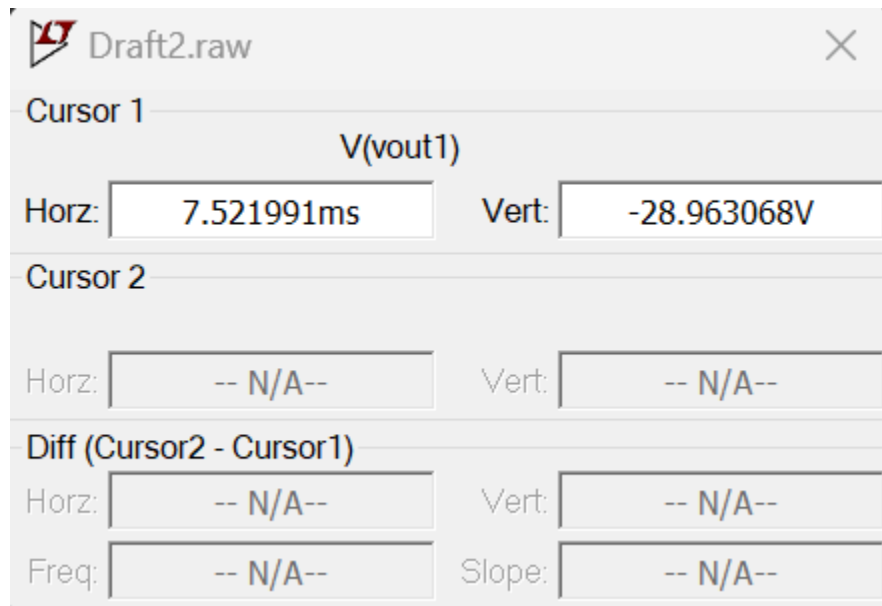

Based on the experiment, $V_{out} = -28.96 \text{ V}$, $V_d = 10 \text{ V}$

$-28.96 = -10(D/1-D) \rightarrow D = 0.74 \rightarrow$ **Step up voltage**

$V_{out 2} = 30.51$

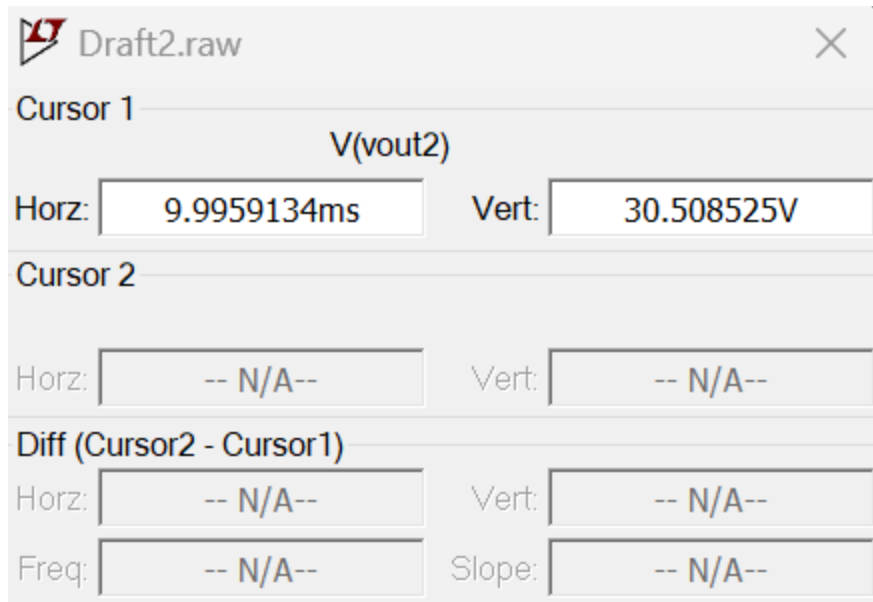

$30.51 = -10(D/1-D) \rightarrow D = 1.49 \rightarrow$ **step up voltage**

6)



Theory:

6)

$$(2.1) \quad V_o = -V_d \frac{D}{1-D}$$

$$(2.3) \quad I_L = \frac{V_d D}{R(1-D)^2}$$

When D=25

$$V_o = -10(25/1-25) = 10.42$$

When D=50

$$V_o = -10(50/1-50) = 10.20$$

When D=75

$$V_o = -10(75/1-75) = 10.135$$

Finding IL

When D= 25

$$I_L = V_d D / R(1-D)^2 = 10 * 25 / (15 * (1-25)^2) = 0.029 \text{ A}$$

When D=50

$$I_L = V_d D / R(1-D)^2 = 10 * 50 / (15 * (1-50)^2) = 0.014 \text{ A}$$

When D=75

$$I_L = V_d D / R(1-D)^2 = 10 * 75 / (15 * (1-75)^2) = 0.009 \text{ A}$$

7)

When D= 25:

$$I_{\text{ripple}} = I_L * V_{\text{out}} / V_{\text{in}} = 0.029 \text{ A} * (10.42 / 10) = 0.03 \text{ (A)}$$

When D= 50:

$$I_{\text{ripple}} = I_L * V_{\text{out}} / V_{\text{in}} = 0.014 \text{ A} * (10.20 / 10) = 0.02958 \text{ (A)}$$

When D= 75:

$$I_{\text{ripple}} = I_L * V_{\text{out}} / V_{\text{in}} = 0.009 \text{ A} * (10.135 / 10) = 9.1215 * 10^{-3} \text{ (A)}$$

8) Comparison between using the switching and average dynamic models:

Overall, the difference between

Switching model:

- +Captures detailed transient responses, including all high-frequency components and oscillations. This level of detail is crucial for designing and testing the control system's reaction to rapid changes.


- +Essential for precise, detailed analysis, such as studying switch stress, transient responses, and optimizing component-level efficiency.

Average Dynamic Model:

- +Great for designing systems and developing control strategies. It provides quick insights into overall behavior and stability without the heavy computation required for detailed switching simulations.

PART 3:

Schematic:

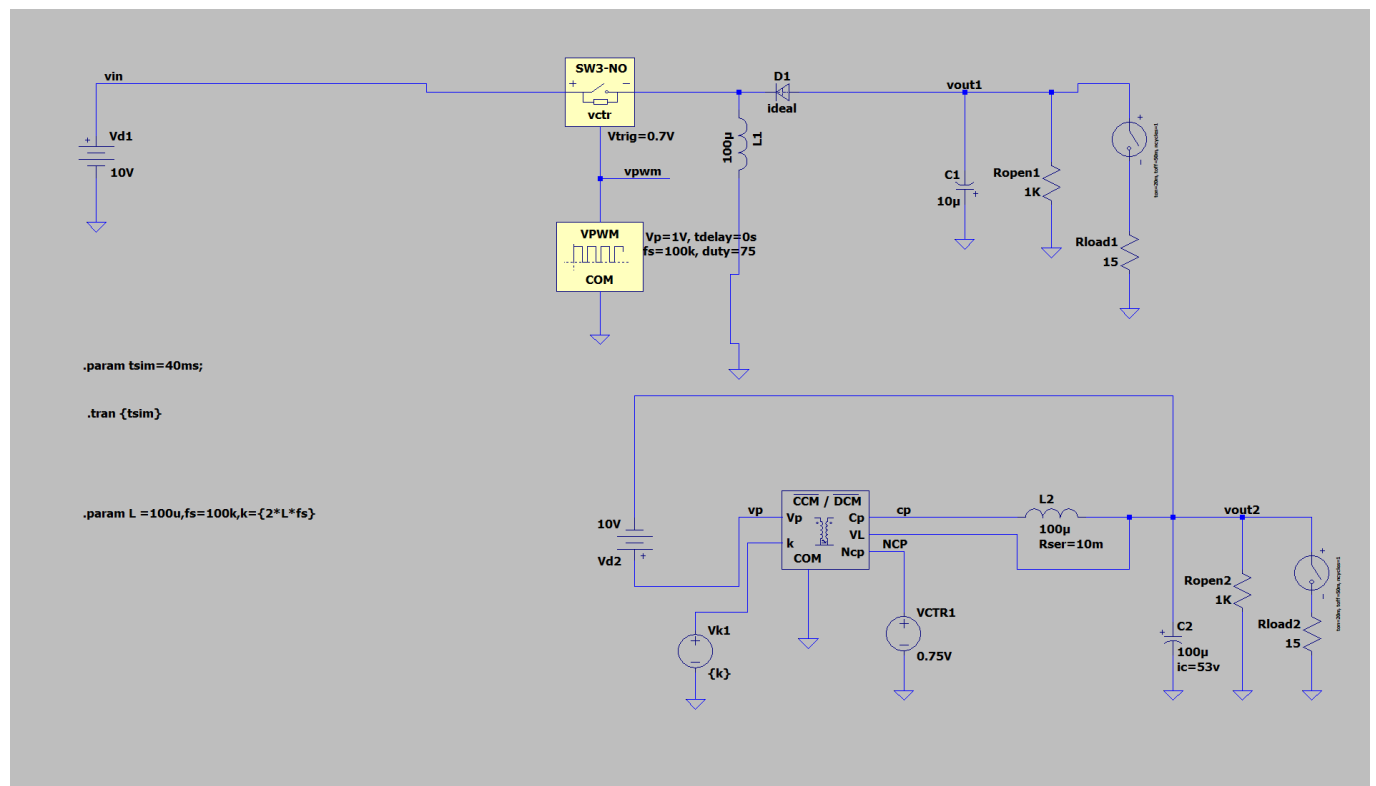



6)

The problem why the output are not stable because the transient time, the overshoot current from the inductance IL1 and IL2. For the transient time, IL1 and IL2 oscillates rapidly when the load is changed. For the current overshoot, the current is higher than the steady state current. Because of that, the output is not stabilized.



7)

After deleting the switching model:

```
.param tsim=40ms;
```


```
.tran {tsim}
```
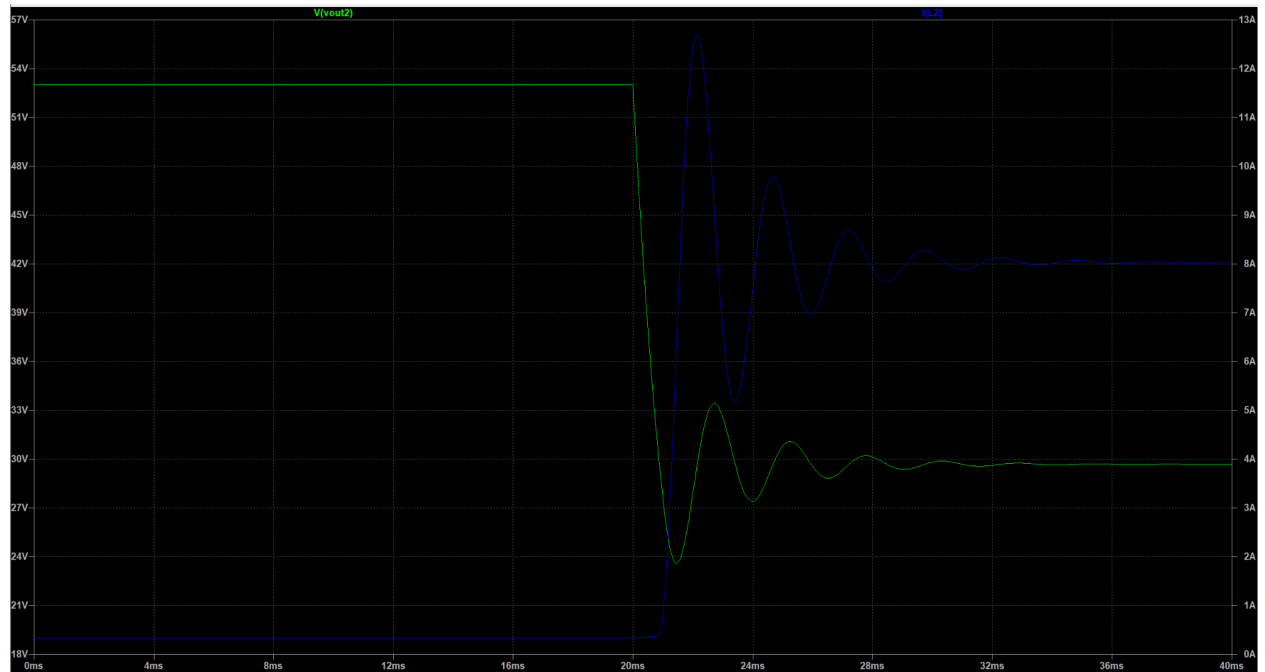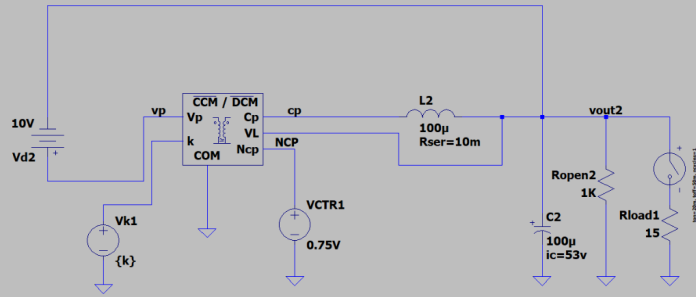
```
.param L =100u,fs=100k,k={2*L*fs}
```




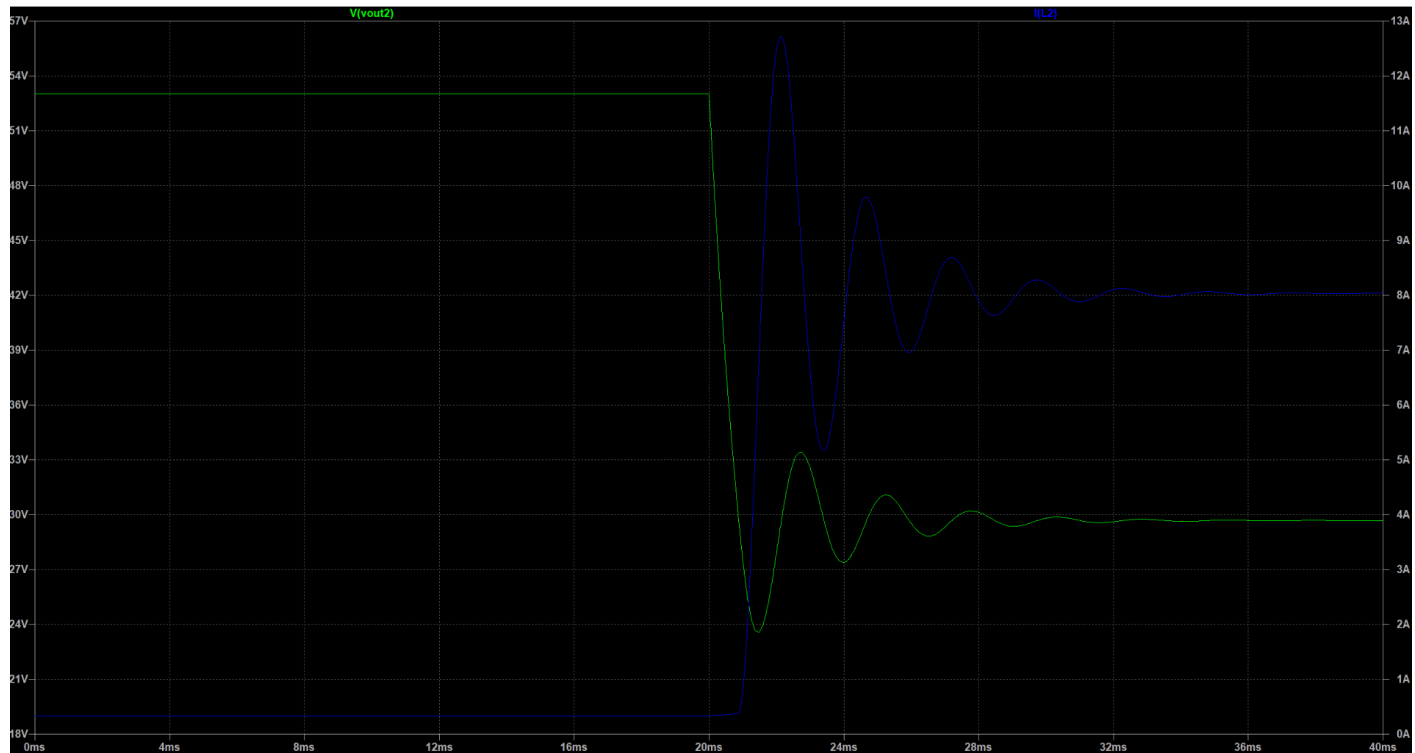8)

With portion containing the switch model:



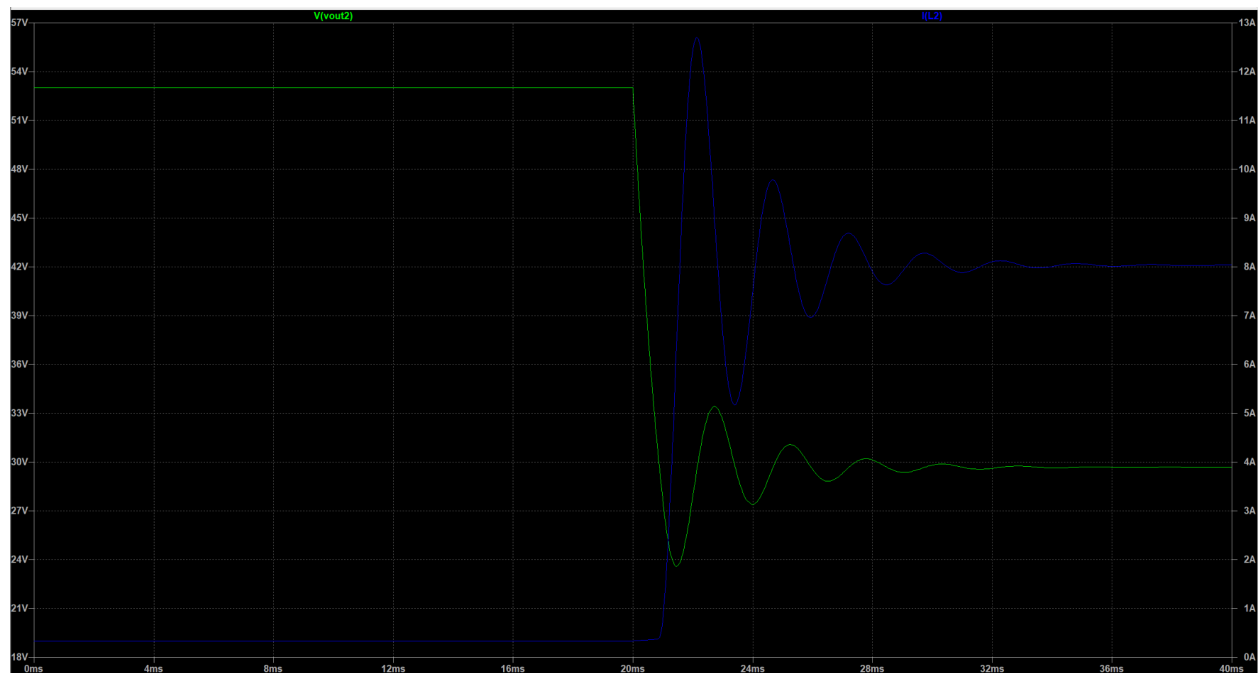Without portion containing the switch model



The time it takes for obtaining the average switching model has similar time it takes with portion containing the switch model.

Practice Problem Encounters:

A problem we encountered is that during part 1, we mistakenly used 10V for V_d . We realized it after we had finished all of our calculations. For part 1, we used resistor values 10, 80, 100, and 500 rather than the given 10, 50, 80, and 500 which resulted in our answers differing from our peers. We did do all the same calculations and processes so our resulting conclusions stayed the same.

Conclusion:

We successfully understood the principles of operation of buck and buck-boost DC-DC converters. We learned how discontinuous current mode (DCM) affects converters. We now know how to design DC-DC converters that operate in continuous current mode (CCM). We learned how the non-linear switching operation can be replaced by the linear average CCM-DCM modeling, and its advantages and disadvantages. We understand the need for system feedback control in the design/development of switch-mode regulators. Even though some of our variable values were wrong we still ended up with the same conclusions due to our calculations and processes being the same.